

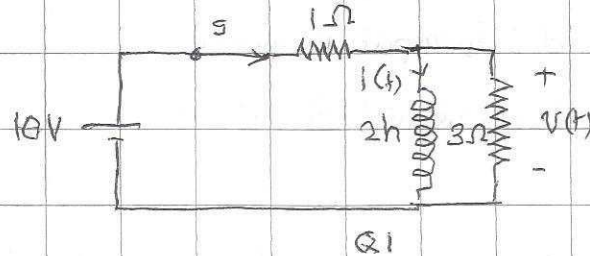


ASSIGNMENT 4

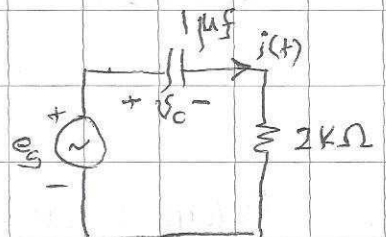Q1 Switch S is closed until steady state is reached and then opened. Assuming it is opened at $t=0$, find $i(t)$ and $v(t)$ for $t > 0$




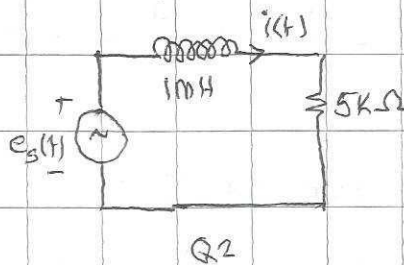Q2 : Let $i(0) = 2\text{mA}$. The source $e_s(t)$ is made ^{DC} 10V for $t > 0$ and current $i_{10}(t)$ is noted. Then $e_s(t)$ is made ^{DC} 30V for $t > 0$ and current $i_{30}(t)$ is measured. Is $i_{30}(t) = 3 i_{10}(t)$. Why? If $i(0) = 0$, and the same experiment is conducted with $i_{30}(t) = 3 i_{10}(t)$. Why?



Q3 : Let $v_c(0) = 1\text{V}$. The source e_s puts out $30\cos(2\pi \times 10^3 t + \phi)$. calculate $i(t)$ for $t \geq 0$. Is there a value of ϕ such that the complete response $i(t)$ does not have any transients?

Q4

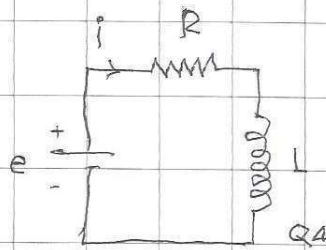

$$R = 500 \Omega \quad L = 10 \text{ mH} \quad e = 8 \text{ V}$$

$$i(0) = -10 \text{ mA}$$

- calculate $i(t)$ $t \geq 0$ by computing zero-state
- response and zero input response
- Is there a steady state value of $i(t)$?

Q5

Given a network N containing R, L and C . The zero-state response $v_1(t)$ to the sinusoidal input $i_1(t) = \cos 2t$ for $t \geq 0$ is given by


$$v_1(t) = e^{-t} + 2e^{-2t} + \cos(2t + 60^\circ) \quad t \geq 0$$

The complete response for $i_2(t) = 3\cos 2t$ $t \geq 0$ when the circuit starts from certain initial state is:

$$v_2(t) = -e^{-t} + 3e^{-2t} + 3\cos(2t + 60^\circ) \quad t \geq 0$$

Determine complete response for $i_3(t) = 5\cos 2t$ $t \geq 0$ if the circuit starts from same initial state.

Q6 !

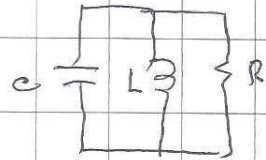


$$\omega_0 = 10 \text{ rad/sec} \quad C = 1 \text{ f} \quad Q = \frac{1}{2}$$

- a. Write down the differential equation governing v_C across capacitor and solve for $v_C(t)$ for $t \geq 0$ for zero input response if $v_C(0) = 2 \text{ volts}$ and $i_L(0) = 5 \text{ amp}$.

- b. Now connect a current source $i_s(t) = \cos 2t$ $t \geq 0$ in parallel to the network.

Initial conditions are same.

Find the complete response

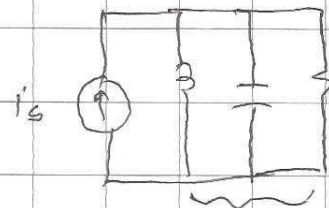

Same as in (a)

- c. Can you separate zero state response from the complete response?

