

MAHINDRA ECOLE CENTRAL

EE101 INTRODUCTION TO ELECTRICAL ENGINEERING  
FIRST SEMESTER 2014-15

ASSIGNMENT 2

QUESTION 1. A resistive circuit driven by a current source is shown in Fig 1.

- i. Draw the oriented graph denoting the edges as numbered in the Figure
- ii. Answer the following with respect to the graph:
  - a. Are 12, 123, 23, 34, 13, 234 trees? Give reasons
  - b. Are 123, 234, 14, 124, circuits? Give reasons
- iii. Write the complete incidence matrix  $A_c$ . Take node c as the reference node and write the reduced incidence matrix A.
- iv. Taking 34 as the tree write down the fundamental circuit matrix  $B_f$
- v. Check  $AB_f^T = 0$
- vi. Write KCL equations using A
- vii. Write KVL equations using  $B_f$
- viii. Find all currents through and voltages across the network elements  $R_2 = 2$  ohms,  $R_3 = 3$  ohms and  $R_4 = 4$  ohms and also the current source assume  $I = 1$  amp
- ix. Check Tellegen's Theorem
- x. Now remove the current source and replace it by a voltage source  $E_s$  of 1 volt. Repeat Viii and IX
- xi. Change  $R_2 = 4$  ohms,  $R_3 = 2$  ohms and  $R_4 = 1$  ohm and repeat viii with voltage source  $E_s$  of 1 volt
- xii. Now we have three sets of voltages and currents as per viii, x, xi. Take a voltage set from one and current set from any other and show that Tellegen is valid!

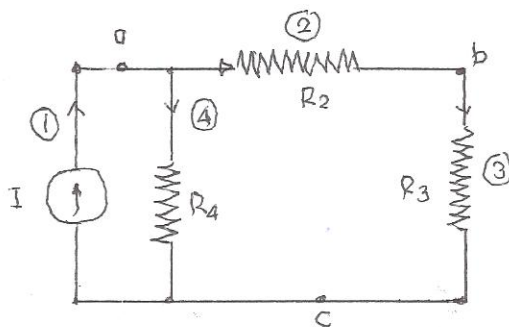


FIG 1

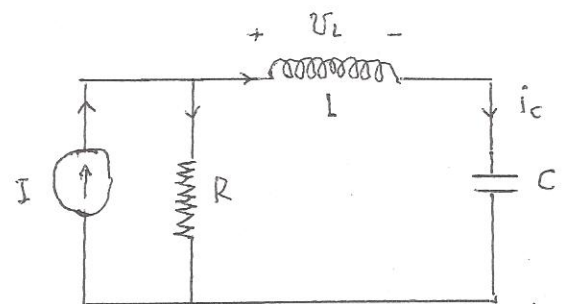


FIG 2

(assume zero initial condition)