

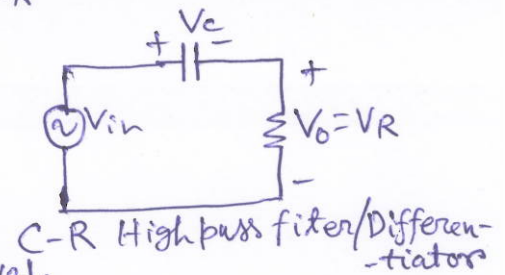


R-C Low pass filter/Integrator

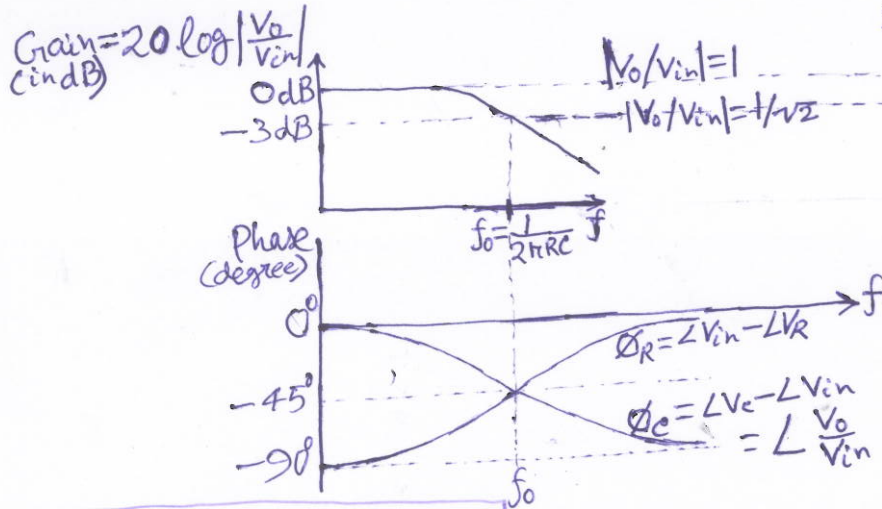

C-R High pass filter/Differentiator

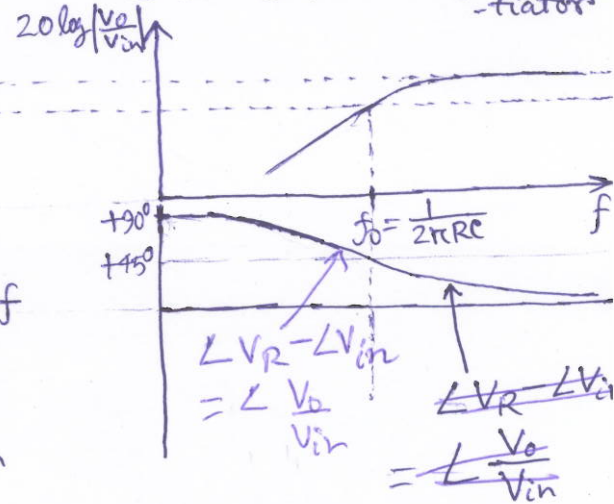

* e.g. $I = 4.12 \sin \omega t$, $\angle I = \angle V_R = \omega t$
 $V_{in} = 5 \sin(\omega t - 57^\circ)$
 $\angle V_{in} = \omega t - 57^\circ$
 $\therefore \angle V_R = \angle V_{in} - \angle V_c = -57^\circ$



Phasor diagram at different frequency

$I = 0, V_R = 0$

at $f = 0$ (DC)

at $f < f_0$ (i.e. $RC \ll T$)


Gain (R-C) = $\left| \frac{V_c}{V_{in}} \right| \approx 1$
 Gain (C-R) = $\left| \frac{V_R}{V_{in}} \right| \ll 1$
 C-R works as differentiator
 i.e. $V_o = V_R = RC \frac{dV_{in}}{dt}$

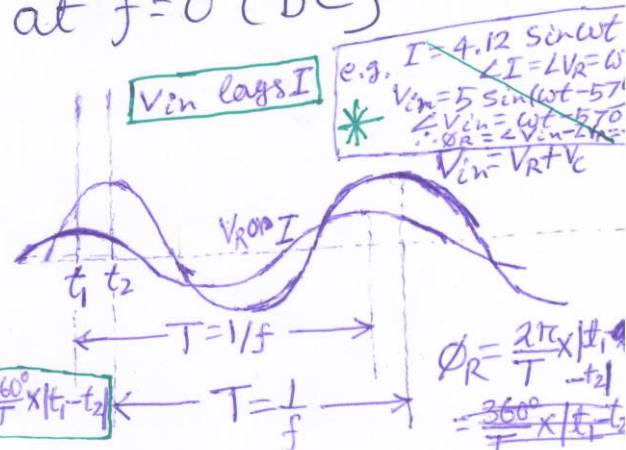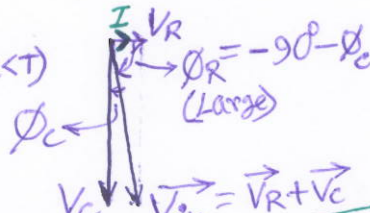

Increase frequency, $V_c \rightarrow 0, V_R \uparrow, \phi_R \rightarrow 0^\circ$

at $f \gg f_0$ (i.e. $RC \gg T$)

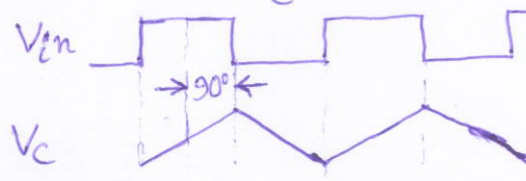Gain (C-R) ≈ 1
 Gain (R-C) $\ll 1$, R-C works as Integrator, i.e. $V_o = V_c = \frac{1}{RC} \int V_{in} dt$
 $\angle V_c - \angle V_{in} \approx -90^\circ$



at $f = \infty$

