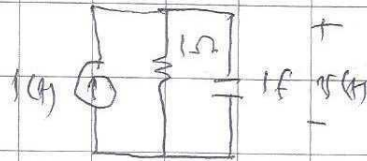


ASSIGNMENT 5

Q1




$$i(t) = 1 + 2 \cos 2t$$

find steady state $v(t)$

Q2


$$e(t) = 50 \sin(10t + \pi/4)$$

$$i(t) = 400 \cos(10t + \pi/6)$$

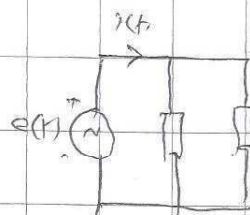

find suitable elements R or L or C and their values.


Q3

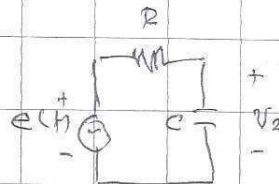

$$e(t) = \cos \omega t$$

find R and C which will make $v_2(t)$ lag 45° behind $e(t)$. What is magnitude of $v_2(t)$ at that frequency.

Q4

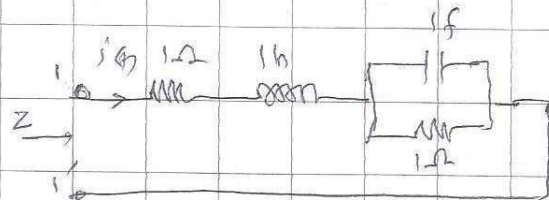

• Determine $Z(j\omega)$. Plot magnitude and phase for $0 < \omega < \infty$

• If $v_s(t) = 10 \cos 2t$ is applied between 1 and 1'


what is current $i(t)$ into the network

• If a current source $i_s(t) = 1 + \cos t + \cos 2t$ is applied at 1, 1'

determine steady state voltage $v(t)$ across 2, 2'

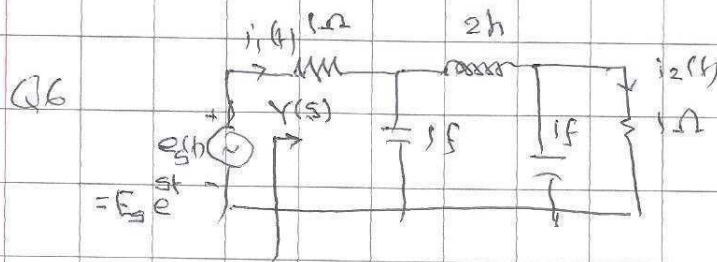Q5. The change of $Z(j\omega) = R(\omega) + jX(\omega)$ as ω varies from 0 to ∞ is plotted on argand diagram with $R(\omega)$ on x-axis and $X(\omega)$ on y-axis (imaginary axis) (Real axis)

For the problem in Q4, what is the locus of impedance i.e. (at $\omega = \omega$, calculate $R(\omega)$ and $X(\omega)$ plot the complex number $Z(j\omega)$ on argand diagram. change $0 < \omega < \infty$ and draw the locus)




a. Calculate $Y(s)$

b. calculate $\frac{I_2(s)}{E_s} = Y_2(s)$


c. If $e_s(t) = 2\cos 2t$, find $i_1(t)$ and $i_2(t)$

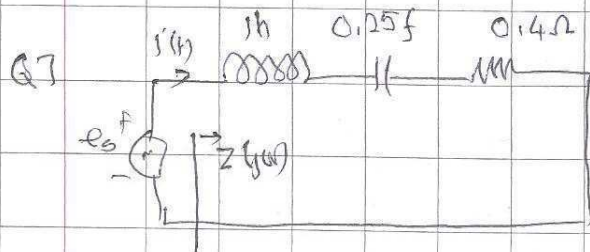d. Do you observe any commonality between $Y(s)$ and $Y_2(s)$. If so, can you argue why it is so?



- Find $i(t)$ if $e_s = \sin \omega t$
- for $\omega = 2, 2.02, 2.04 \text{ rad/sec}$

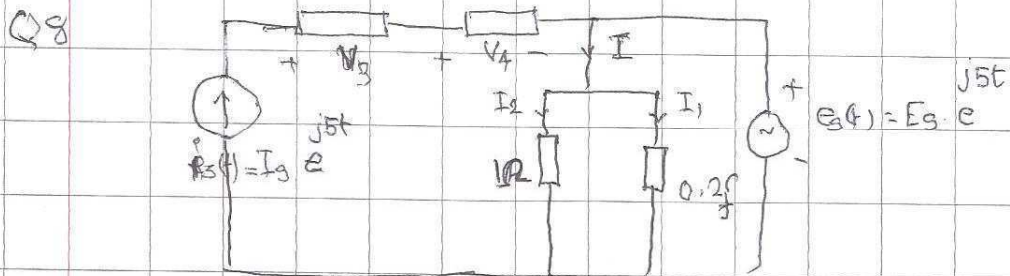- calculate average energy stored in capacitor at above ω s
- calculate average energy stored in inductor at above ω s
- calculate the average power dissipated at above ω s
- Is there any relation between $Z(j\omega)$ and the average stored energies and dissipated power at these ω s




- It is found $I = I_0 e^{j5t + j\theta}$ with $I_0 = 10\sqrt{2}$
- What is E_0 and θ

- It is found $V_4 = 1 \angle 0^\circ$ and $V_5 = 2\sqrt{2} \angle 90^\circ$ for $I_0 = 1 \text{ amp}$
- What are the elements corresponding to V_4 and V_5

- Find complex power in all elements and sources and separate real power and reactive power
- Does average power supplied = average power dissipated
- compute average energy stored in storage elements

Q9

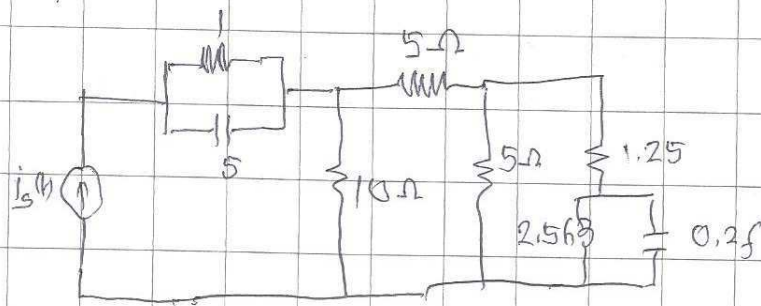

$$i_s(t) = 10 \cos t$$

Find all voltages across and currents through all elements in the network compute at the input terminals P_{av} and Q_{av} and check $\sum_{\text{all elements}} P_{av_i} = P_{av_{\text{input}}}$

(you may use Thevenin/Norton for simplifying calculations)