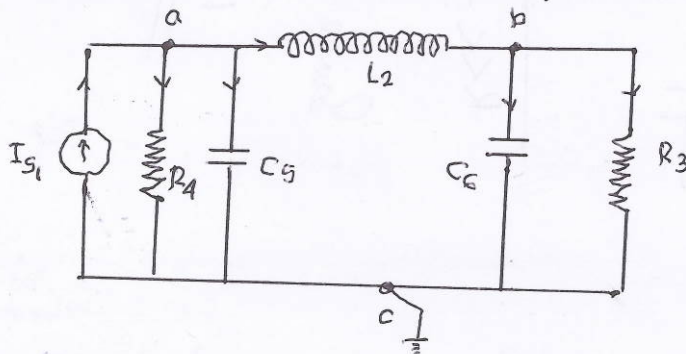


MAHINDRA ECOLE CENTRAL

EE 101 INTRODUCTION TO ELECTRICAL ENGINEERING First Semester 2014-2015

ASSIGNMENT 3

1. Solve the following network by node and mesh analysis. Assume zero initial conditions on inductors and capacitors



2*. Assuming that the initial conditions are zero, solve the following network by node and mesh analysis method. The controlled voltage source is a voltage source whose value of voltage is K times the value of the node voltage V_b which is same as the voltage across the capacitor C_4 . Note the asymmetry in the matrix relating node voltages with the current excitation and similarly the matrix relating mesh currents to the current excitation.

