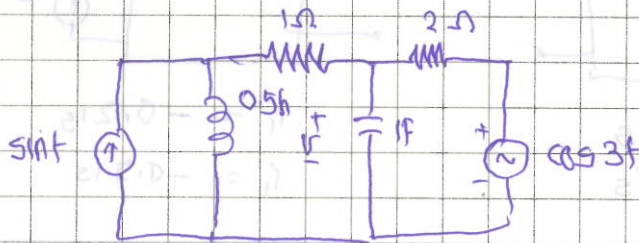


Q1 Using Superposition Theorem find  $v(t)$  in steady state



Q2: Solve the same problem in Q1 by state-space methods. Assume network is in zero state with no initial values.


Q3 The network is in sinusoidal steady state

$$e_s(t) = 9 \cos 10t \quad i_s(t) = 2 \cos(10t - \pi/3)$$

(a) Find Thevenin equivalent of network to the left of AB


(b) Find Norton equivalent "

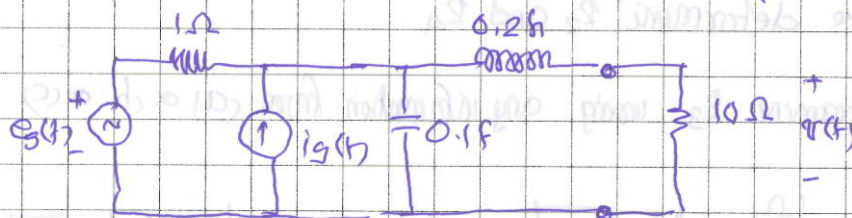(c) calculate  $v(t)$  with the use of Thevenin equivalent.




$e_s(t)$  and  $i_s(t)$  are as given above

Q4

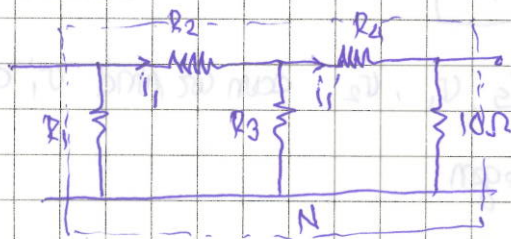


solo

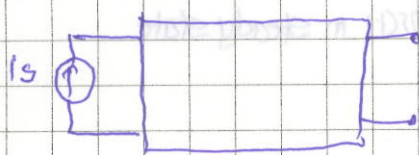(a) Two measurements are made for  $i_1$  and  $i_1'$  as shown in figs below



$$i_1 = 0.6 i_s$$

$$i_1' = 0.3 i_s$$

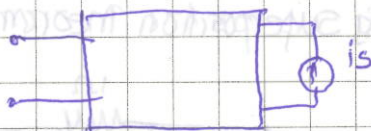


$$i_1 = -0.2 i_s$$

$$i_1' = -0.9 i_s$$

Find  $R_1$  using Tellegen's theorem.

(b)

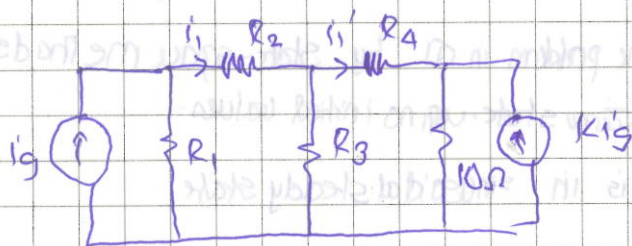

What is the value of  $K$  to make current in  $R_3$  zero.



Use  $R_1$  from (a)

(c) With the value of  $K$  in (b), find  $i_1$  and  $i_1'$  ( $= i_1$ )

hence determine  $R_2$  and  $R_4$

(d) determine  $R_3$  using any information from (a) or (b) or (c)

Q5:


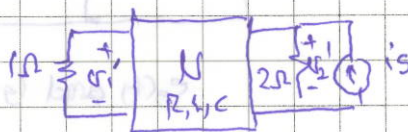
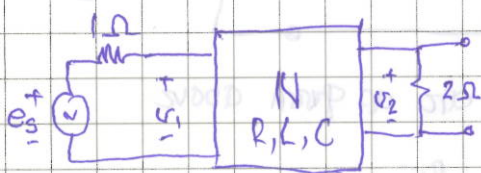


given  $e_s$ ,  $i_s$ ,  $v_1$ ,  $v_2$  can we find  $v_1'$  and  $v_2'$

using Tellegen.




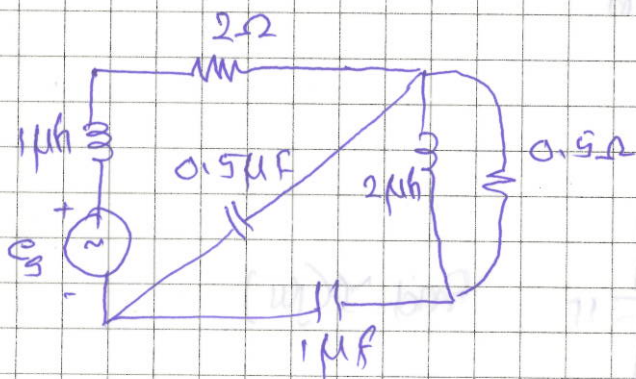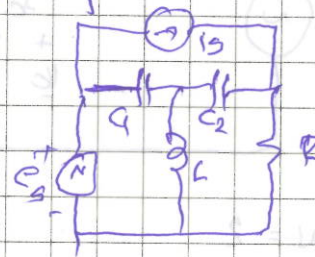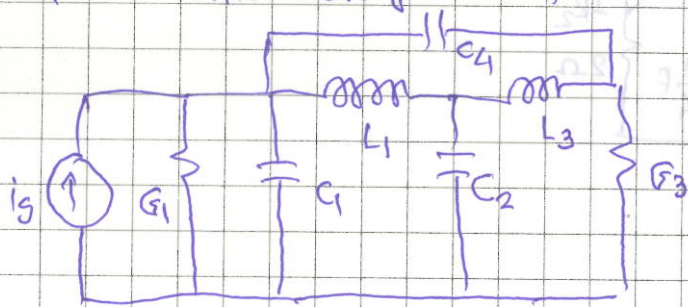Q6: Write state equations for the following networks:



(Do not try to solve)  
for the state)


Q7:

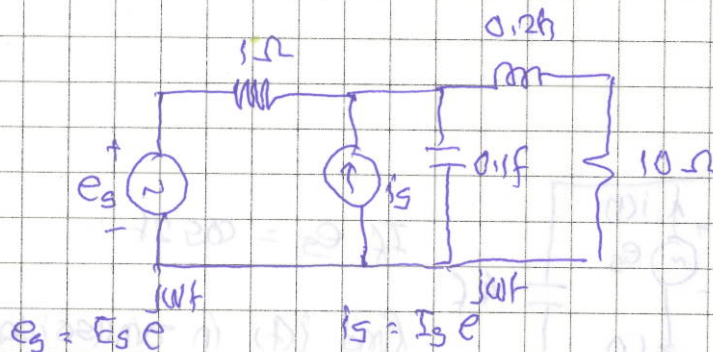

$$e_3 = E_s e^{j\omega t}$$

$$i_5 = I_s e^{j\omega t}$$

Draw the phasor diagram for the network.

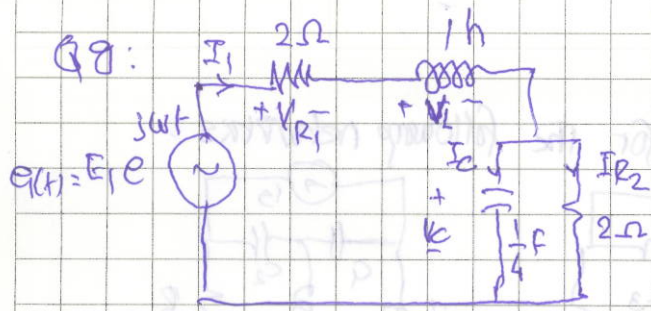

Draw the phasor diagram

