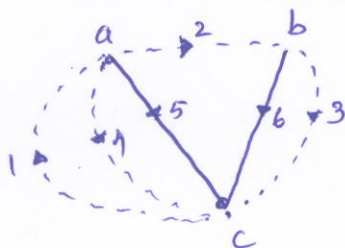


EE101 Assignment-3 Solutions.

1



Proper tree, oriented graph.

Node Analysis

$$A = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 \end{matrix} \\ \begin{matrix} a \\ b \end{matrix} & \begin{bmatrix} -1 & 1 & 0 & 1 & 1 & 0 \\ 0 & -1 & 1 & 0 & 0 & 1 \end{bmatrix} \end{matrix}$$

Step 1:

$$A i_b = 0$$

$$\Rightarrow \begin{bmatrix} -1 & 1 & 0 & 1 & 1 & 0 \\ 0 & -1 & 1 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_{b1} \\ i_{b2} \\ i_{b3} \\ i_{b4} \\ i_{b5} \\ i_{b6} \end{bmatrix} = 0$$

But $i_{b1} = I_s$, So taking it separate

$$\begin{bmatrix} 1 & 0 & 1 & 1 & 0 \\ -1 & 1 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_{b2} \\ i_{b3} \\ i_{b4} \\ i_{b5} \\ i_{b6} \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \end{bmatrix} I_s \quad \text{--- (1)}$$

Step 2:

$$\begin{bmatrix} i_{b2} \\ i_{b3} \\ i_{b4} \\ i_{b5} \\ i_{b6} \end{bmatrix} = \begin{bmatrix} \frac{1}{L_2} & 0 & 0 & 0 & 0 \\ 0 & \frac{1}{R_3} & 0 & 0 & 0 \\ 0 & 0 & \frac{1}{R_4} & 0 & 0 \\ 0 & 0 & 0 & C & 0 \\ 0 & 0 & 0 & 0 & C \end{bmatrix} \begin{bmatrix} v_{b2} \\ v_{b3} \\ v_{b4} \\ v_{b5} \\ v_{b6} \end{bmatrix}$$

where $D \Rightarrow \frac{d}{dt}$
 $D^{-1} \Rightarrow \int dt$.

(1)

Step: 3

$$V_b = A^T \cdot V_n$$

$$\begin{bmatrix} V_{b1} \\ V_{b2} \\ V_{b3} \\ V_{b4} \\ V_{b5} \\ V_{b6} \end{bmatrix} = \begin{bmatrix} -1 & 0 \\ 1 & -1 \\ 0 & 1 \\ 1 & 0 \\ 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \end{bmatrix}$$

V_{b1} is the voltage across current source. Hence we need to express it in terms of other node voltages. From the matrix

$$\boxed{V_{b1} = -V_a}$$

$$\begin{bmatrix} V_{b2} \\ V_{b3} \\ V_{b4} \\ V_{b5} \\ V_{b6} \end{bmatrix} = \begin{bmatrix} 1 & -1 \\ 0 & 1 \\ 1 & 0 \\ 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \end{bmatrix}$$

Step-4

Substituting in

(1)


$$\begin{bmatrix} 1 & 0 & 1 & 1 & 0 \\ -1 & 1 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} \frac{1}{L_2} D^{-1} & 0 & 0 & 0 & 0 \\ 0 & \frac{1}{R_3} & 0 & 0 & 0 \\ 0 & 0 & \frac{1}{R_4} & 0 & 0 \\ 0 & 0 & 0 & C_5 D & 0 \\ 0 & 0 & 0 & 0 & C_6 D \end{bmatrix} \begin{bmatrix} 1 & -1 \\ 0 & 1 \\ 1 & 0 \\ 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \end{bmatrix} I_s$$

$$\Rightarrow \begin{bmatrix} \frac{1}{L_2} D^{-1} & 0 & \frac{1}{R_4} & C_5 D & 0 \\ -\frac{1}{L_2} D^{-1} & \frac{1}{R_3} & 0 & 0 & C_6 D \end{bmatrix} \begin{bmatrix} 1 & -1 \\ 0 & 1 \\ 1 & 0 \\ 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \end{bmatrix} I_s$$

$$\Rightarrow \begin{bmatrix} \frac{1}{L_2} D^{-1} + \frac{1}{R_4} + C_5 D & -\frac{1}{L_2} D^{-1} \\ -\frac{1}{L_2} D^{-1} & \frac{1}{L_2} D^{-1} + C_6 D + \frac{1}{R_3} \end{bmatrix} \begin{bmatrix} V_a \\ V_b \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \end{bmatrix} I_s$$

(2)

Mesh Analysis

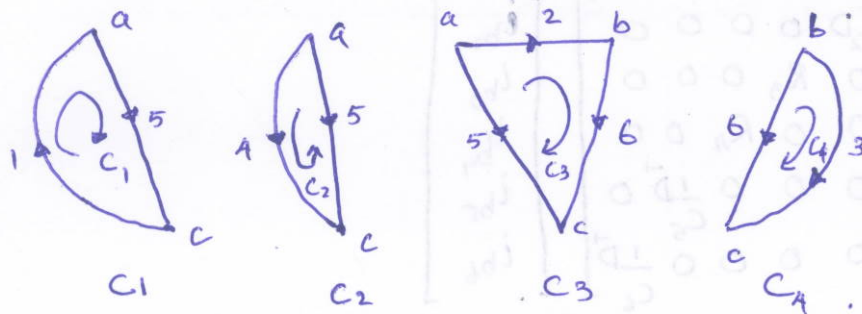

Step 1.

$$B = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 \end{matrix} \\ \begin{matrix} C_1 \\ C_2 \\ C_3 \\ C_4 \end{matrix} & \begin{bmatrix} 1 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 & -1 & 0 \\ 0 & 1 & 0 & 0 & 0 & -1 \\ 0 & 0 & 1 & 0 & 0 & -1 \end{bmatrix} \end{matrix}$$

$$BV_b = 0$$

$$\Rightarrow \begin{bmatrix} 1 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 & -1 & 0 \\ 0 & 1 & 0 & 0 & 0 & -1 \\ 0 & 0 & 1 & 0 & 0 & -1 \end{bmatrix} \begin{bmatrix} V_{b1} \\ V_{b2} \\ V_{b3} \\ V_{b4} \\ V_{b5} \\ V_{b6} \end{bmatrix} = 0.$$

Now V_{b1} is a current source. Since we don't have $v-i$ relation for it, we need to eliminate it. From the matrix

$$V_{b1} + V_{b5} = 0$$

$$\text{or } \boxed{V_{b1} = -V_{b5}}$$

Now we can remove first row or B matrix. Now the first column is all zeros, which enables us to remove the first column along with V_{b1} .

$$\begin{bmatrix} 0 & 0 & 1 & -1 & 0 \\ 1 & 0 & 0 & -1 & 1 \\ 0 & 1 & 0 & 0 & -1 \end{bmatrix} \begin{bmatrix} V_{b2} \\ V_{b3} \\ V_{b4} \\ V_{b5} \\ V_{b6} \end{bmatrix} = 0. \quad \text{--- (1)}$$

(3)

Step-2.

$$\begin{bmatrix} V_{b2} \\ V_{b3} \\ V_{b4} \\ V_{b5} \\ V_{b6} \end{bmatrix} = \begin{bmatrix} L_2 D & 0 & 0 & 0 & 0 \\ 0 & R_3 & 0 & 0 & 0 \\ 0 & 0 & R_4 & 0 & 0 \\ 0 & 0 & 0 & \frac{1}{C_5} D^{-1} & 0 \\ 0 & 0 & 0 & 0 & \frac{1}{C_6} D^{-1} \end{bmatrix} \begin{bmatrix} i_{b2} \\ i_{b3} \\ i_{b4} \\ i_{b5} \\ i_{b6} \end{bmatrix}$$

Step-3.

$$I_b = B^T I_m$$

$$\begin{bmatrix} i_{b1} \\ i_{b2} \\ i_{b3} \\ i_{b4} \\ i_{b5} \\ i_{b6} \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 1 & 0 & 0 \\ 1 & -1 & -1 & 0 \\ 0 & 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} I_{m1} \\ I_{m2} \\ I_{m3} \\ I_{m4} \end{bmatrix}$$

$$\text{But } I_{m1} = I_s,$$

$$\Rightarrow I_{b1} = I_s,$$

$$\begin{bmatrix} i_{b2} \\ i_{b3} \\ i_{b4} \\ i_{b5} \\ i_{b6} \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \\ -1 & -1 & 0 \\ 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} i_{m2} \\ i_{m3} \\ i_{m4} \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 0 \\ 1 \\ 0 \end{bmatrix} I_s$$

Step-4

Now substituting in (1).

$$\begin{bmatrix} 0 & 0 & 1 & -1 & 0 \\ 1 & 0 & 0 & -1 & 1 \\ 0 & 1 & 0 & 0 & -1 \end{bmatrix} \begin{bmatrix} L_2 D & 0 & 0 & 0 & 0 \\ 0 & R_3 & 0 & 0 & 0 \\ 0 & 0 & R_4 & 0 & 0 \\ 0 & 0 & 0 & \frac{1}{C_5} D^{-1} & 0 \\ 0 & 0 & 0 & 0 & \frac{1}{C_6} D^{-1} \end{bmatrix} \begin{bmatrix} i_{m2} \\ i_{m3} \\ i_{m4} \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 0 \\ 1 \\ 0 \end{bmatrix} I_s$$

$$\begin{bmatrix} 0 & 0 & R_4 & -\frac{1}{C_5} D^{-1} & 0 \\ L_2 D & 0 & 0 & -\frac{1}{C_5} D^{-1} & \frac{1}{C_6} D^{-1} \\ 0 & R_3 & 0 & 0 & -\frac{1}{C_6} D^{-1} \end{bmatrix} \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \\ -1 & -1 & 0 \\ 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} i_{m2} \\ i_{m3} \\ i_{m4} \end{bmatrix} + \begin{bmatrix} 0 & 0 & 0 \\ L_2 D & 0 & 0 \\ 0 & R_3 & 0 \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ 1 \\ 1 \\ 0 \end{bmatrix} I_s$$

$$\begin{bmatrix} R_4 + \frac{1}{C_5} D^{-1} & \frac{1}{C_5} D^{-1} & 0 \\ \frac{1}{C_5} D^{-1} & L_2 D + \frac{1}{C_5} D^{-1} + \frac{1}{C_6} D^{-1} & -\frac{1}{C_6} D^{-1} \\ 0 & -\frac{1}{C_6} D^{-1} & R_3 + \frac{1}{C_6} D^{-1} \end{bmatrix} \begin{bmatrix} i_{m2} \\ i_{m3} \\ i_{m4} \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 0 \\ \frac{1}{C_5} D^{-1} \\ 0 \end{bmatrix} I_s = 0$$

$$\begin{bmatrix} R_4 + \frac{1}{C_5} D^{-1} & \frac{1}{C_5} D^{-1} & 0 \\ \frac{1}{C_5} D^{-1} & L_2 D + \frac{1}{C_5} D^{-1} + \frac{1}{C_6} D^{-1} & -\frac{1}{C_6} D^{-1} \\ 0 & -\frac{1}{C_6} D^{-1} & R_3 + \frac{1}{C_6} D^{-1} \end{bmatrix} \begin{bmatrix} i_{m2} \\ i_{m3} \\ i_{m4} \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ -\frac{1}{C_5} D^{-1} \\ 0 \end{bmatrix} I_s$$

②. This question you can solve in the same way. Let's try applying KCL and KVL, whether we can get the same answer.

1. Node analysis.

Applying KCL at node 'a'.

$$-I_s + \frac{V_a}{R_2} + \frac{V_a - V_b}{R_3} + \frac{d(V_a - V_c)}{5 dt} = 0$$

But V_c is given as KV_b .

$$-I_s + \frac{V_a}{R_2} + \frac{V_a - V_b}{R_3} + C_5 D (V_a - KV_b) = 0 \quad \text{--- (1)}$$

Applying KCL at node 'b'

$$-\frac{(V_a - V_b)}{R_3} + C D V_b = 0 \quad \text{--- (2)}$$

At node c, we already know $V_c = KV_b$. --- (3)

Now writing equations 1 and 2 in matrix format

$$\begin{bmatrix} \frac{1}{R_2} + \frac{1}{R_3} + C_5 D & -\frac{1}{R_3} - K C_5 D \\ -\frac{1}{R_3} & \frac{1}{R_3} + C D \end{bmatrix} \begin{bmatrix} V_a \\ V_b \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \end{bmatrix} I_s$$


$$V_c = K V_b$$

This is the required solution.




See the Matrix is asymmetric. Check Q1 answer. It is symmetric.

Mesh Analysis

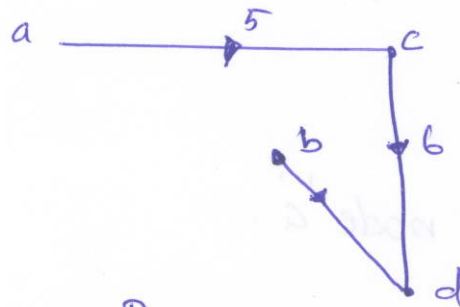Again we try with KVL to see whether we get the same answer.



Proper tree.

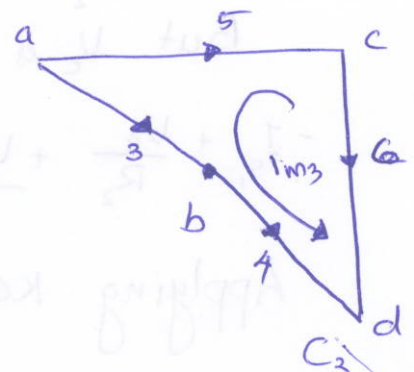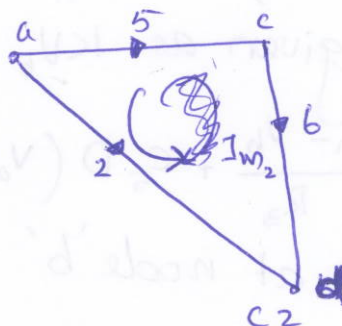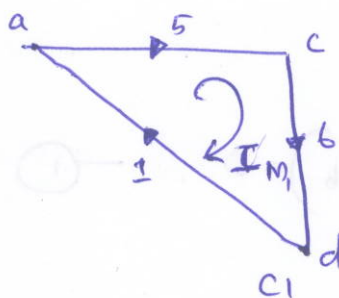

Circuits.

Now writing KVL for each circuit,

From C_1 , $I_{m1} = I_s$, - (1)

From C_2 ,

$$\frac{1}{C_5} \frac{dI_{m1}}{dt} + \frac{1}{C_5} \frac{dI_{m2}}{dt} + \frac{1}{R_2} I_{m2} - K V_b = \frac{1}{C_5} \frac{dI_{m2}}{dt} = 0 \quad (6)$$

$$-\frac{1}{C_5} \bar{D}' \begin{bmatrix} I_{s_1} & -I_{m_2} & -I_{m_3} \end{bmatrix} + I_{m_2} R_2 - e_{s_6} = 0$$

$$e_{s_6} = K V_b.$$

$$\text{But } V_b = \frac{1}{C_4} \bar{D}' I_{m_3} \quad (\text{from } C_3)$$

$$-\frac{1}{C_5} \bar{D}' I_{s_1} + \frac{1}{C_5} \bar{D}' I_{m_2} + \frac{1}{C_5} \bar{D}' I_{m_3} + I_{m_2} R_2 - \frac{1}{C_4} \bar{D}' I_{m_3} = 0 \quad (2)$$

From C_3

$$I_{m_3} R_3 - \frac{1}{C_4} \bar{D}' I_{m_3} - K \frac{1}{C_4} \bar{D}' I_{m_3} - \frac{1}{C_5} \bar{D}' (I_{s_1} - I_{m_2} - I_{m_3}) = 0 \quad (3)$$

Writing equations (2) and (3) in matrix format

$$\begin{bmatrix} \frac{1}{C_5} \bar{D}' + R_2 & \frac{1}{C_5} \bar{D}' - \frac{1}{C_4} \bar{D}' \\ \frac{1}{C_5} \bar{D}' & R_3 - \frac{1}{C_4} \bar{D}' - \frac{K \bar{D}'}{C_4} + \frac{1}{C_5} \bar{D}' \end{bmatrix} \begin{bmatrix} I_{m_2} \\ I_{m_3} \end{bmatrix} = \begin{bmatrix} +\frac{1}{C_5} \bar{D}' \\ \frac{1}{C_5} \bar{D}' \end{bmatrix} I_{s_1}$$

$$\underline{\underline{I_{m_1} = I_{s_1}}}$$