

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

10: Sine waves and phasors

Sine Waves

10: Sine waves and phasors

- Sine Waves

- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

For inductors and capacitors $i = C \frac{dv}{dt}$ and $v = L \frac{di}{dt}$ so we need to differentiate $i(t)$ and $v(t)$ when analysing circuits containing them.

Sine Waves


10: Sine waves and phasors

● Sine Waves

- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

For inductors and capacitors $i = C \frac{dv}{dt}$ and $v = L \frac{di}{dt}$ so we need to differentiate $i(t)$ and $v(t)$ when analysing circuits containing them.

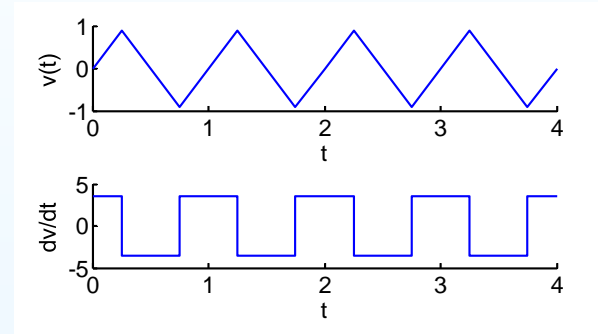Usually differentiation changes the shape of a waveform.



Sine Waves

10: Sine waves and phasors

● Sine Waves


- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

For inductors and capacitors $i = C \frac{dv}{dt}$ and $v = L \frac{di}{dt}$ so we need to differentiate $i(t)$ and $v(t)$ when analysing circuits containing them.

Usually differentiation changes the shape of a waveform.

For bounded waveforms there is only one exception:
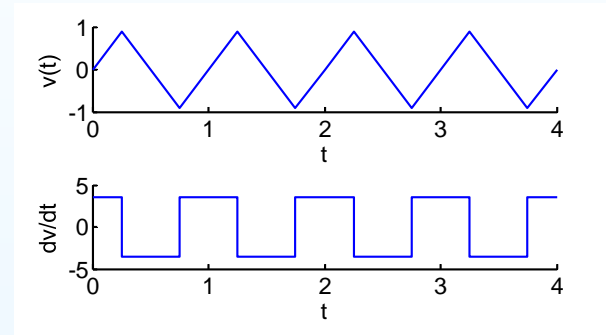
$$v(t) = \sin t \Rightarrow \frac{dv}{dt} = \cos t$$



Sine Waves

10: Sine waves and phasors

● Sine Waves





- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

For inductors and capacitors $i = C \frac{dv}{dt}$ and $v = L \frac{di}{dt}$ so we need to differentiate $i(t)$ and $v(t)$ when analysing circuits containing them.

Usually differentiation changes the shape of a waveform.

For bounded waveforms there is only one exception:
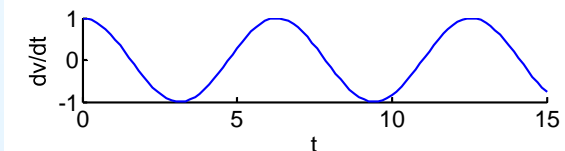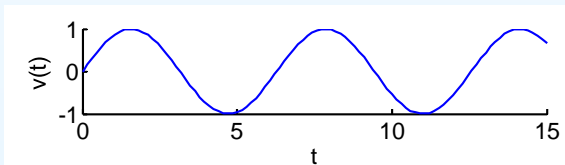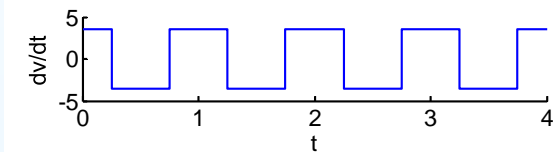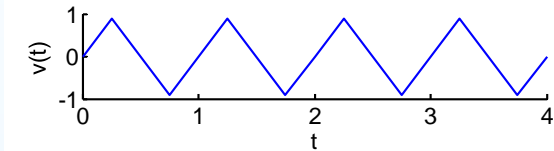
$$v(t) = \sin t \Rightarrow \frac{dv}{dt} = \cos t$$



Sine Waves

10: Sine waves and phasors

● Sine Waves



- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

For inductors and capacitors $i = C \frac{dv}{dt}$ and $v = L \frac{di}{dt}$ so we need to differentiate $i(t)$ and $v(t)$ when analysing circuits containing them.

Usually differentiation changes the shape of a waveform.

For bounded waveforms there is only one exception:

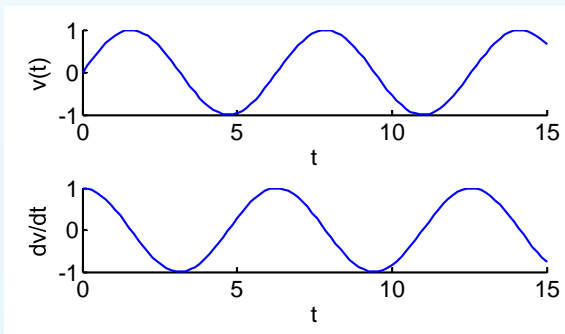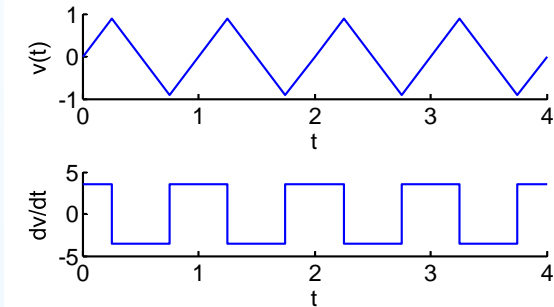$v(t) = \sin t \Rightarrow \frac{dv}{dt} = \cos t$
same shape but with a time shift.



Sine Waves

10: Sine waves and phasors

● Sine Waves

- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)





For inductors and capacitors $i = C \frac{dv}{dt}$ and $v = L \frac{di}{dt}$ so we need to differentiate $i(t)$ and $v(t)$ when analysing circuits containing them.

Usually differentiation changes the shape of a waveform.

For bounded waveforms there is only one exception:

$v(t) = \sin t \Rightarrow \frac{dv}{dt} = \cos t$
same shape but with a time shift.

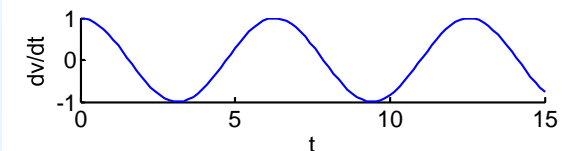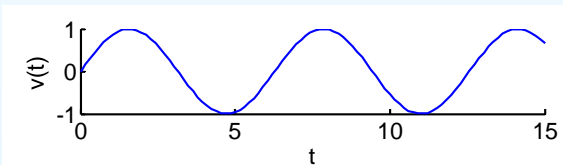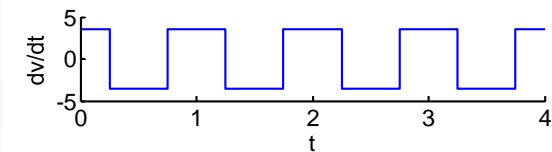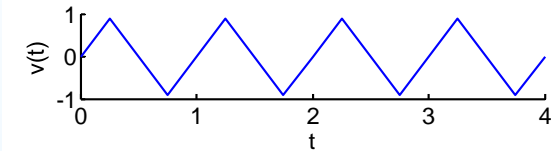$\sin t$ completes one full period every time t increases by 2π .



Sine Waves

10: Sine waves and phasors

● Sine Waves

- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

For inductors and capacitors $i = C \frac{dv}{dt}$ and $v = L \frac{di}{dt}$ so we need to differentiate $i(t)$ and $v(t)$ when analysing circuits containing them.





Usually differentiation changes the shape of a waveform.

For bounded waveforms there is only one exception:

$v(t) = \sin t \Rightarrow \frac{dv}{dt} = \cos t$
same shape but with a time shift.

$\sin t$ completes one full period every time t increases by 2π .

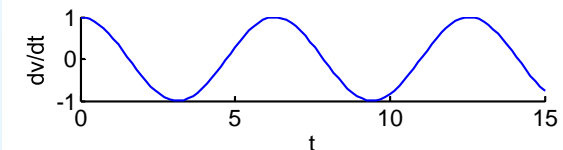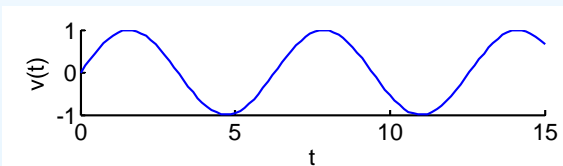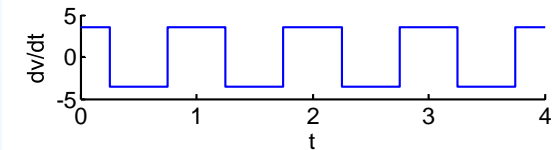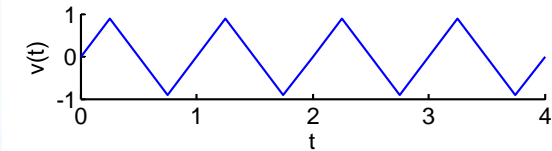$\sin 2\pi ft$ makes f complete repetitions every time t increases by 1; this gives a **frequency** of f cycles per second, or f Hz.



Sine Waves

10: Sine waves and phasors

● Sine Waves

- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

For inductors and capacitors $i = C \frac{dv}{dt}$ and $v = L \frac{di}{dt}$ so we need to differentiate $i(t)$ and $v(t)$ when analysing circuits containing them.

Usually differentiation changes the shape of a waveform.

For bounded waveforms there is only one exception:



$v(t) = \sin t \Rightarrow \frac{dv}{dt} = \cos t$
same shape but with a time shift.

$\sin t$ completes one full period every time t increases by 2π .

$\sin 2\pi ft$ makes f complete repetitions every time t increases by 1; this gives a **frequency** of f cycles per second, or f Hz.

We often use the **angular frequency**, $\omega = 2\pi f$ instead.

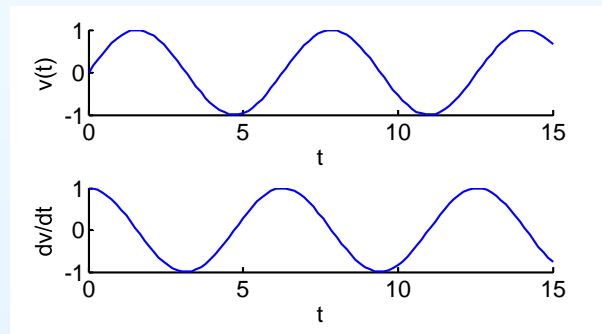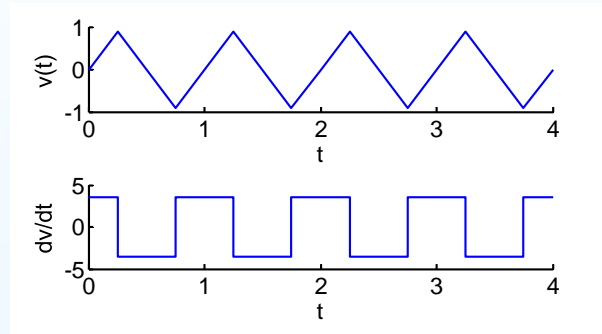ω is measured in **radians per second**. E.g. $50 \text{ Hz} \simeq 314 \frac{\text{rad}}{\text{s}}$.




10: Sine waves and phasors

- Sine Waves
- **Rotating Rod**
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Rotating Rod

A useful way to think of a cosine wave is as the projection of a rotating rod onto the horizontal axis.

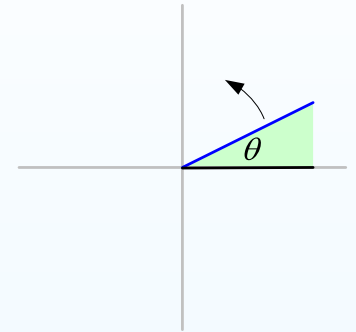For a unit-length rod, the projection has length $\cos \theta$.



10: Sine waves and phasors

- Sine Waves
- **Rotating Rod**
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)


Rotating Rod

A useful way to think of a cosine wave is as the projection of a rotating rod onto the horizontal axis.

For a unit-length rod, the projection has length $\cos \theta$.

If the rod is rotating at a speed of f revolutions per second, then θ increases uniformly with time:

$$\theta = 2\pi ft.$$

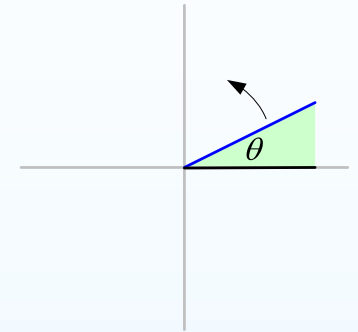

10: Sine waves and phasors

- Sine Waves
- **Rotating Rod**
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Rotating Rod


A useful way to think of a cosine wave is as the projection of a rotating rod onto the horizontal axis.

For a unit-length rod, the projection has length $\cos \theta$.

If the rod is rotating at a speed of f revolutions per second, then θ increases uniformly with time:

$$\theta = 2\pi ft.$$

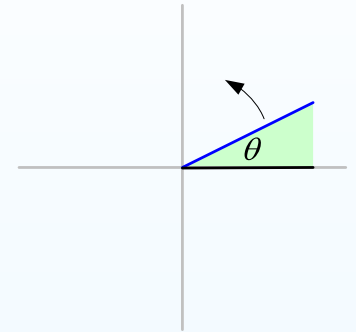The only difference between \cos and \sin is the starting position of the rod:



10: Sine waves and phasors

- Sine Waves
- **Rotating Rod**
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Rotating Rod



A useful way to think of a cosine wave is as the projection of a rotating rod onto the horizontal axis.

For a unit-length rod, the projection has length $\cos \theta$.

If the rod is rotating at a speed of f revolutions per second, then θ increases uniformly with time:

$$\theta = 2\pi ft.$$

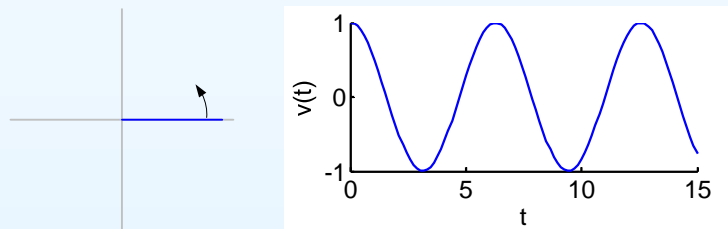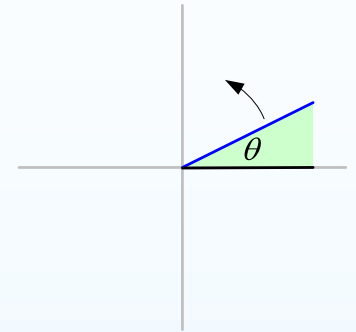The only difference between \cos and \sin is the starting position of the rod:



$$v = \cos 2\pi ft$$

Rotating Rod

10: Sine waves and phasors

- Sine Waves
- **Rotating Rod**
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)




A useful way to think of a cosine wave is as the projection of a rotating rod onto the horizontal axis.

For a unit-length rod, the projection has length $\cos \theta$.



If the rod is rotating at a speed of f revolutions per second, then θ increases uniformly with time:

$$\theta = 2\pi ft.$$

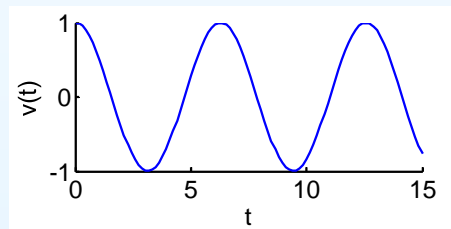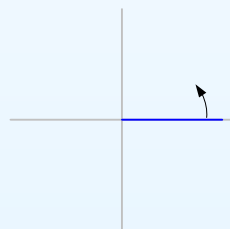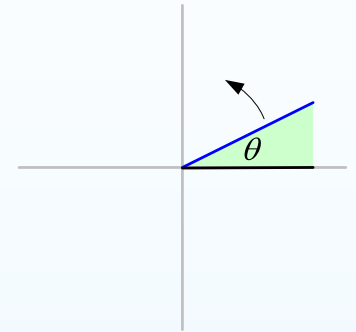The only difference between \cos and \sin is the starting position of the rod:



$$v = \cos 2\pi ft$$

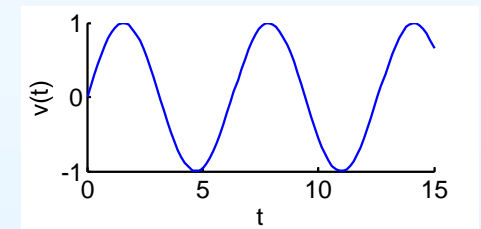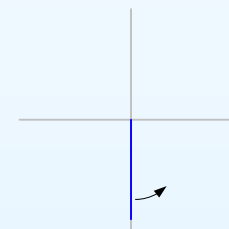

$$v = \sin 2\pi ft$$

Rotating Rod

10: Sine waves and phasors

- Sine Waves
- **Rotating Rod**
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)




A useful way to think of a cosine wave is as the projection of a rotating rod onto the horizontal axis.

For a unit-length rod, the projection has length $\cos \theta$.



If the rod is rotating at a speed of f revolutions per second, then θ increases uniformly with time:

$$\theta = 2\pi ft.$$

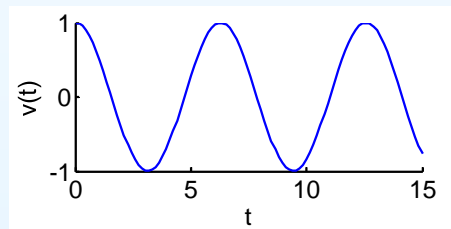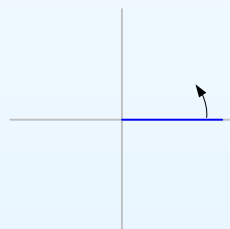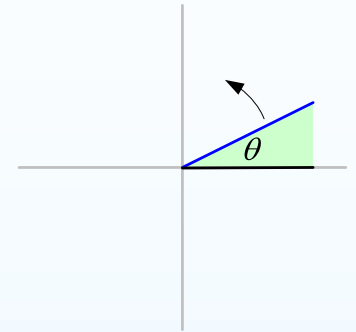The only difference between \cos and \sin is the starting position of the rod:



$$v = \cos 2\pi ft$$

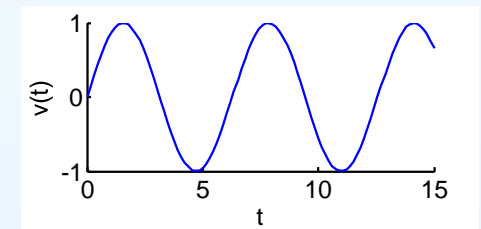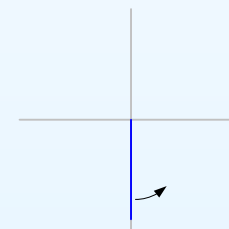

$$v = \sin 2\pi ft = \cos \left(2\pi ft - \frac{\pi}{2} \right)$$

Rotating Rod

10: Sine waves and phasors

- Sine Waves
- **Rotating Rod**
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)




A useful way to think of a cosine wave is as the projection of a rotating rod onto the horizontal axis.

For a unit-length rod, the projection has length $\cos \theta$.



If the rod is rotating at a speed of f revolutions per second, then θ increases uniformly with time:

$$\theta = 2\pi ft.$$

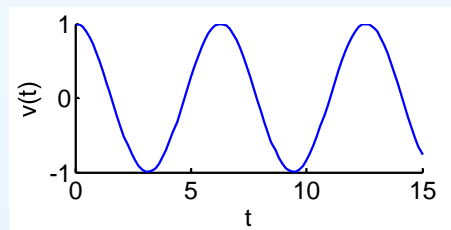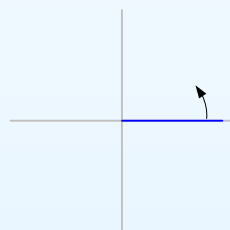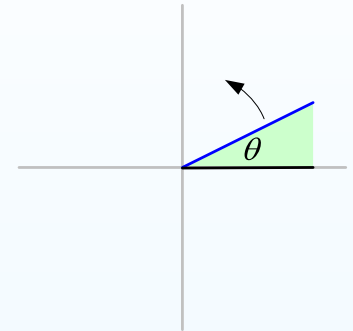The only difference between \cos and \sin is the starting position of the rod:



$$v = \cos 2\pi ft$$

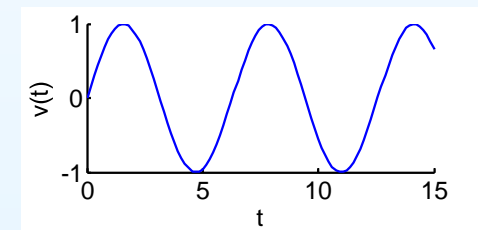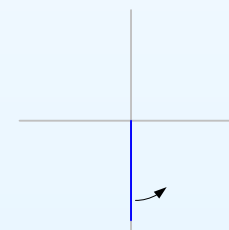

$$v = \sin 2\pi ft = \cos \left(2\pi ft - \frac{\pi}{2} \right)$$

$\sin 2\pi ft$ **lags** $\cos 2\pi ft$ by 90° (or $\frac{\pi}{2}$ radians) because its peaks occurs $\frac{1}{4}$ of a cycle later (equivalently \cos **leads** \sin).


Phasors

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- **Phasors**
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

If the rod has length A and starts at an angle ϕ then the projection onto the horizontal axis is

$$A \cos(2\pi ft + \phi)$$

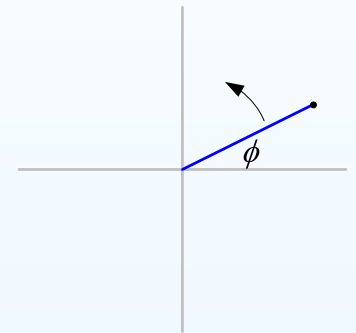


Phasors

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- **Phasors**
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

If the rod has length A and starts at an angle ϕ then the projection onto the horizontal axis is
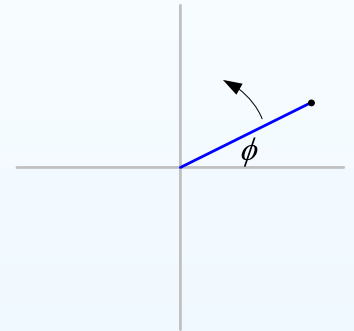
$$\begin{aligned} A \cos(2\pi ft + \phi) \\ = A \cos \phi \cos 2\pi ft - A \sin \phi \sin 2\pi ft \end{aligned}$$




Phasors

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- **Phasors**
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

If the rod has length A and starts at an angle ϕ then the projection onto the horizontal axis is
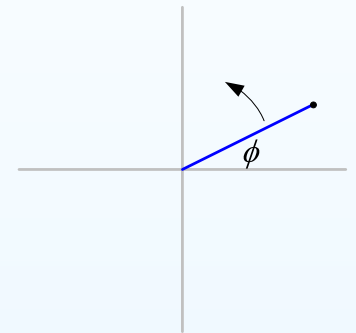
$$\begin{aligned} & A \cos(2\pi ft + \phi) \\ &= A \cos \phi \cos 2\pi ft - A \sin \phi \sin 2\pi ft \\ &= X \cos 2\pi ft - Y \sin 2\pi ft \end{aligned}$$



10: Sine waves and phasors


- Sine Waves
- Rotating Rod
- **Phasors**
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasors

If the rod has length A and starts at an angle ϕ then the projection onto the horizontal axis is

$$\begin{aligned} & A \cos(2\pi ft + \phi) \\ &= A \cos \phi \cos 2\pi ft - A \sin \phi \sin 2\pi ft \\ &= X \cos 2\pi ft - Y \sin 2\pi ft \end{aligned}$$

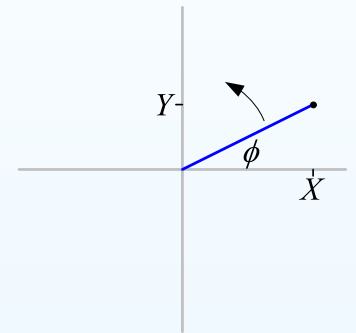At time $t = 0$, the tip of the rod has coordinates (X, Y) .



Phasors

10: Sine waves and phasors


- Sine Waves
- Rotating Rod
- **Phasors**
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

If the rod has length A and starts at an angle ϕ then the projection onto the horizontal axis is

$$\begin{aligned} & A \cos(2\pi ft + \phi) \\ &= A \cos \phi \cos 2\pi ft - A \sin \phi \sin 2\pi ft \\ &= X \cos 2\pi ft - Y \sin 2\pi ft \end{aligned}$$

At time $t = 0$, the tip of the rod has coordinates (X, Y) .

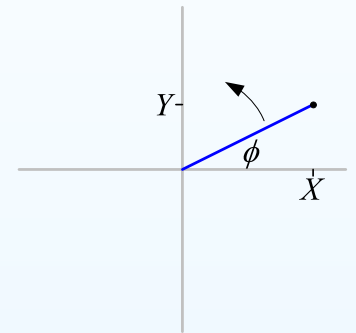If we think of the plane as an Argand Diagram (or complex plane), then the complex number $X + jY$ corresponding to the tip of the rod at $t = 0$ is called a *phasor*.



Phasors


10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- **Phasors**
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

If the rod has length A and starts at an angle ϕ then the projection onto the horizontal axis is

$$\begin{aligned} & A \cos(2\pi ft + \phi) \\ &= A \cos \phi \cos 2\pi ft - A \sin \phi \sin 2\pi ft \\ &= X \cos 2\pi ft - Y \sin 2\pi ft \end{aligned}$$

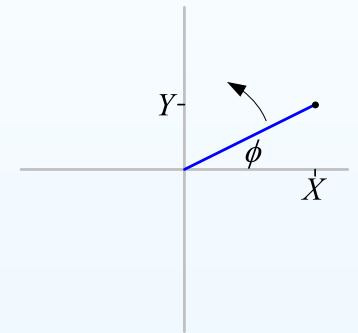At time $t = 0$, the tip of the rod has coordinates (X, Y) .



If we think of the plane as an Argand Diagram (or complex plane), then the complex number $X + jY$ corresponding to the tip of the rod at $t = 0$ is called a *phasor*.

The *magnitude* of the phasor, $A = \sqrt{X^2 + Y^2}$, gives the amplitude (peak value) of the sine wave.


Phasors

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- **Phasors**
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

If the rod has length A and starts at an angle ϕ then the projection onto the horizontal axis is
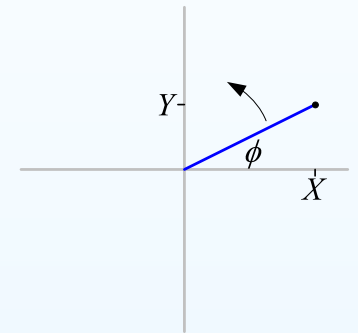
$$\begin{aligned} & A \cos(2\pi ft + \phi) \\ &= A \cos \phi \cos 2\pi ft - A \sin \phi \sin 2\pi ft \\ &= X \cos 2\pi ft - Y \sin 2\pi ft \end{aligned}$$



At time $t = 0$, the tip of the rod has coordinates (X, Y) .

If we think of the plane as an Argand Diagram (or complex plane), then the complex number $X + jY$ corresponding to the tip of the rod at $t = 0$ is called a *phasor*.

The *magnitude* of the phasor, $A = \sqrt{X^2 + Y^2}$, gives the amplitude (peak value) of the sine wave.

The *argument* of the phasor, $\phi = \arctan \frac{Y}{X}$, gives the phase shift relative to $\cos 2\pi ft$.


If $\phi > 0$, it is *leading* and if $\phi < 0$, it is *lagging* relative to $\cos 2\pi ft$.

Phasor Examples

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- **Phasor Examples**
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

$$V = 1, f = 50 \text{ Hz}$$

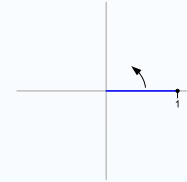


Phasor Examples

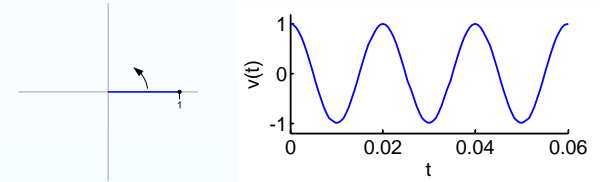10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- **Phasor Examples**
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

$$V = 1, f = 50 \text{ Hz}$$
$$v(t) = \cos 2\pi ft$$



Phasor Examples


10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- **Phasor Examples**
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

$$V = 1, f = 50 \text{ Hz}$$

$$v(t) = \cos 2\pi ft$$

$$V = -j$$

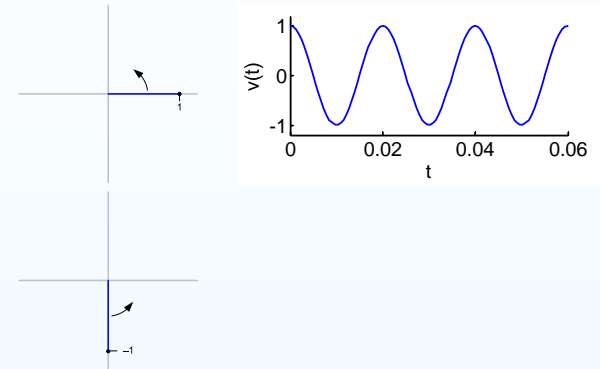

Phasor Examples

10: Sine waves and phasors


- Sine Waves
- Rotating Rod
- Phasors
- **Phasor Examples**
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

$$V = 1, f = 50 \text{ Hz}$$

$$v(t) = \cos 2\pi ft$$

$$V = -j$$

$$v(t) = \sin 2\pi ft$$

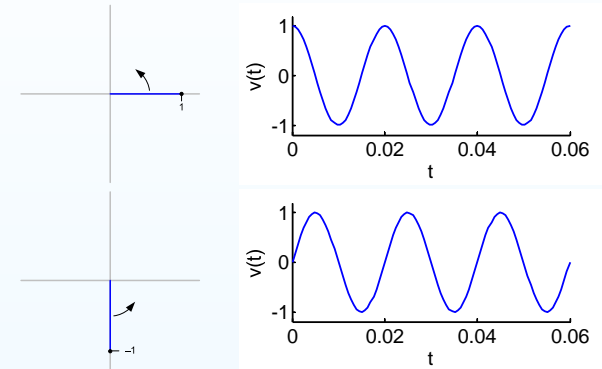

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- **Phasor Examples**
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor Examples


$$V = 1, f = 50 \text{ Hz}$$

$$v(t) = \cos 2\pi ft$$

$$V = -j$$

$$v(t) = \sin 2\pi ft$$

$$V = -1 - 0.5j$$

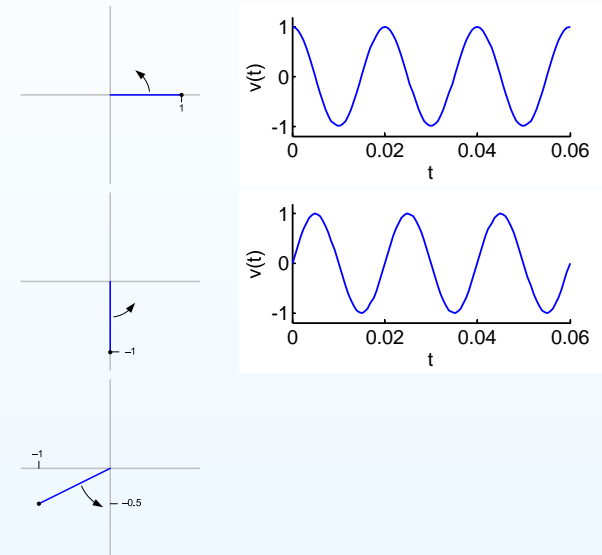

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- **Phasor Examples**
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor Examples

$$V = 1, f = 50 \text{ Hz}$$


$$v(t) = \cos 2\pi ft$$

$$V = -j$$

$$v(t) = \sin 2\pi ft$$

$$V = -1 - 0.5j$$
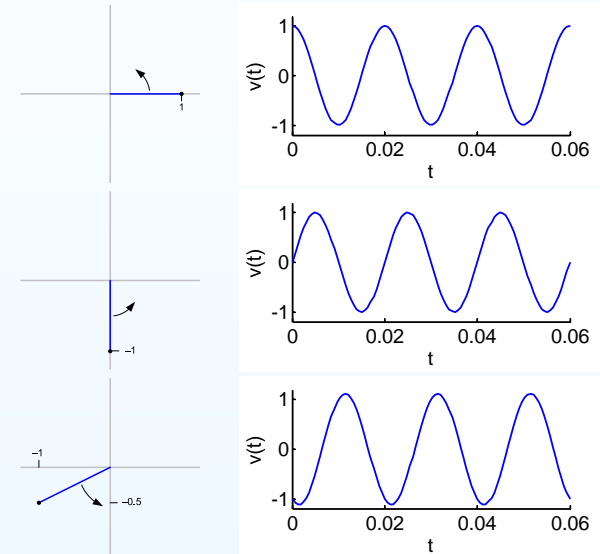
$$v(t) = -\cos 2\pi ft + 0.5 \sin 2\pi ft$$



10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- **Phasor Examples**
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor Examples

$$V = 1, f = 50 \text{ Hz}$$


$$v(t) = \cos 2\pi ft$$

$$V = -j$$

$$v(t) = \sin 2\pi ft$$

$$V = -1 - 0.5j = 1.12 \angle -153^\circ$$
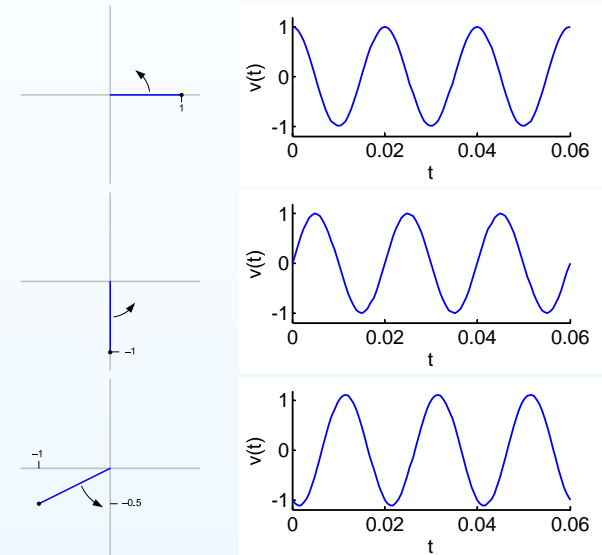
$$v(t) = -\cos 2\pi ft + 0.5 \sin 2\pi ft$$



10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- **Phasor Examples**
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor Examples

$$V = 1, f = 50 \text{ Hz}$$

$$v(t) = \cos 2\pi ft$$


$$V = -j$$

$$v(t) = \sin 2\pi ft$$

$$V = -1 - 0.5j = 1.12 \angle -153^\circ$$

$$v(t) = -\cos 2\pi ft + 0.5 \sin 2\pi ft$$

$$= 1.12 \cos (2\pi ft - 2.68)$$

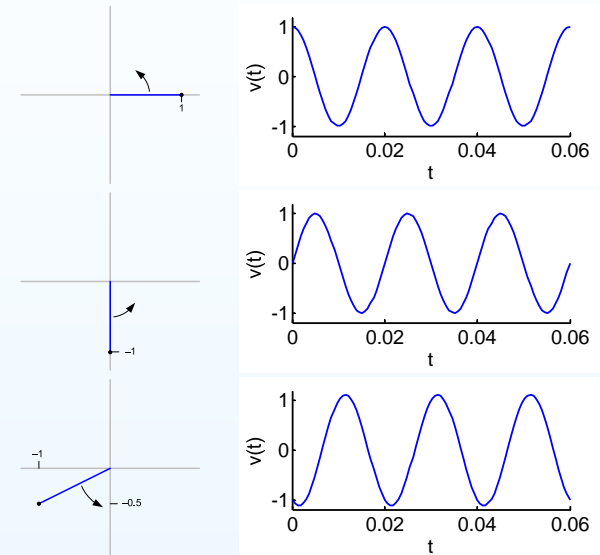

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- **Phasor Examples**
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor Examples

$$V = 1, f = 50 \text{ Hz}$$

$$v(t) = \cos 2\pi ft$$


$$V = -j$$

$$v(t) = \sin 2\pi ft$$

$$V = -1 - 0.5j = 1.12 \angle -153^\circ$$

$$\begin{aligned} v(t) &= -\cos 2\pi ft + 0.5 \sin 2\pi ft \\ &= 1.12 \cos (2\pi ft - 2.68) \end{aligned}$$

$$V = X + jY$$

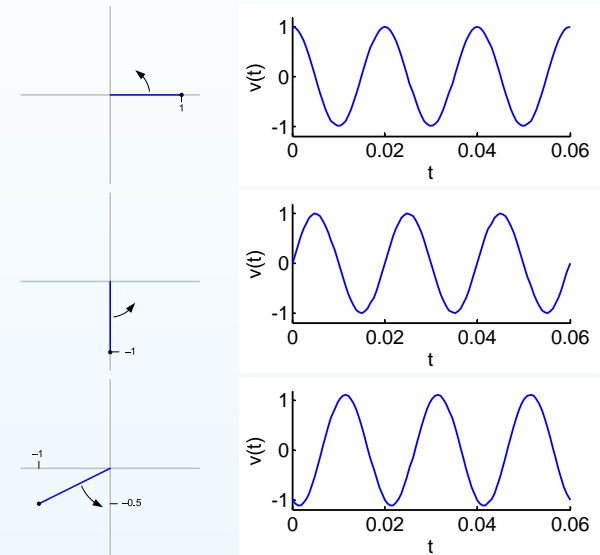

Phasor Examples

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- **Phasor Examples**
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

$$V = 1, f = 50 \text{ Hz}$$

$$v(t) = \cos 2\pi ft$$

$$V = -j$$


$$v(t) = \sin 2\pi ft$$

$$V = -1 - 0.5j = 1.12 \angle -153^\circ$$

$$\begin{aligned} v(t) &= -\cos 2\pi ft + 0.5 \sin 2\pi ft \\ &= 1.12 \cos (2\pi ft - 2.68) \end{aligned}$$

$$V = X + jY$$
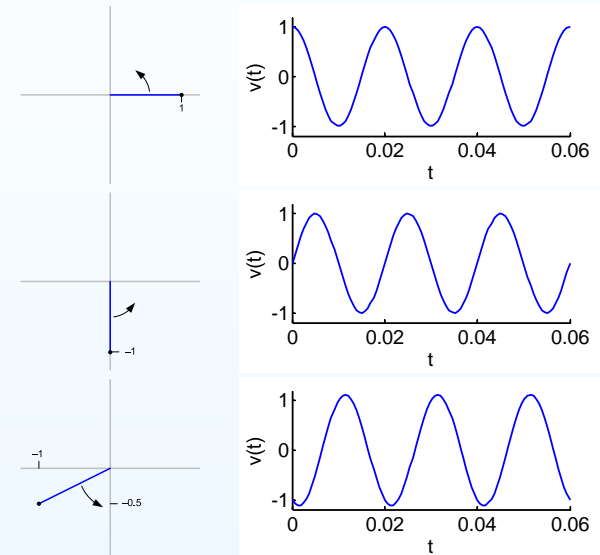
$$v(t) = X \cos 2\pi ft - Y \sin 2\pi ft$$



10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- **Phasor Examples**
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor Examples

$$V = 1, f = 50 \text{ Hz}$$

$$v(t) = \cos 2\pi ft$$

$$V = -j$$

$$v(t) = \sin 2\pi ft$$


$$V = -1 - 0.5j = 1.12 \angle -153^\circ$$

$$\begin{aligned} v(t) &= -\cos 2\pi ft + 0.5 \sin 2\pi ft \\ &= 1.12 \cos (2\pi ft - 2.68) \end{aligned}$$

$$V = X + jY$$

$$v(t) = X \cos 2\pi ft - Y \sin 2\pi ft$$

Beware minus sign.

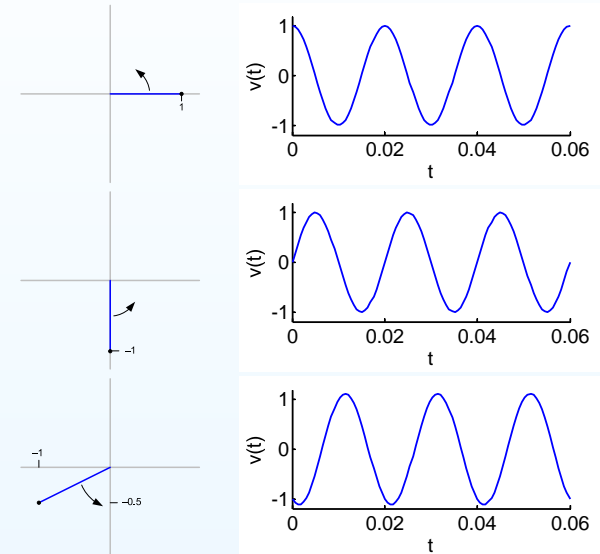

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- **Phasor Examples**
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor Examples

$$V = 1, f = 50 \text{ Hz}$$

$$v(t) = \cos 2\pi ft$$

$$V = -j$$

$$v(t) = \sin 2\pi ft$$


$$V = -1 - 0.5j = 1.12 \angle -153^\circ$$

$$\begin{aligned} v(t) &= -\cos 2\pi ft + 0.5 \sin 2\pi ft \\ &= 1.12 \cos (2\pi ft - 2.68) \end{aligned}$$

$$V = X + jY$$

$$v(t) = X \cos 2\pi ft - Y \sin 2\pi ft$$

Beware minus sign.

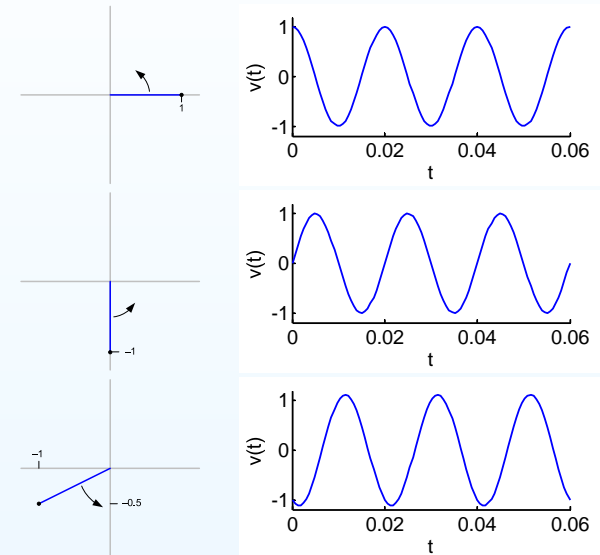

$$V = A \angle \phi$$

Phasor Examples

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- **Phasor Examples**
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

$$V = 1, f = 50 \text{ Hz}$$

$$v(t) = \cos 2\pi ft$$

$$V = -j$$

$$v(t) = \sin 2\pi ft$$

$$V = -1 - 0.5j = 1.12 \angle -153^\circ$$


$$v(t) = -\cos 2\pi ft + 0.5 \sin 2\pi ft$$

$$= 1.12 \cos (2\pi ft - 2.68)$$

$$V = X + jY$$

$$v(t) = X \cos 2\pi ft - Y \sin 2\pi ft$$

Beware minus sign.

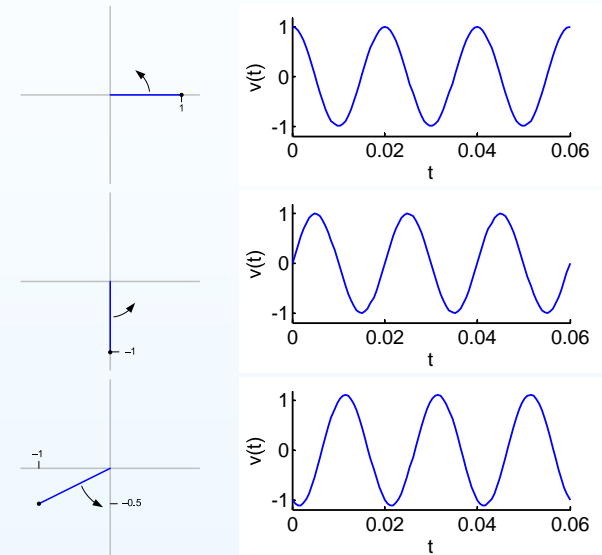

$$V = A \angle \phi$$

$$v(t) = A \cos (2\pi ft + \phi)$$

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- **Phasor Examples**
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor Examples

$$V = 1, f = 50 \text{ Hz}$$

$$v(t) = \cos 2\pi ft$$

$$V = -j$$

$$v(t) = \sin 2\pi ft$$

$$V = -1 - 0.5j = 1.12 \angle -153^\circ$$


$$v(t) = -\cos 2\pi ft + 0.5 \sin 2\pi ft$$

$$= 1.12 \cos (2\pi ft - 2.68)$$

$$V = X + jY$$

$$v(t) = X \cos 2\pi ft - Y \sin 2\pi ft$$

Beware minus sign.

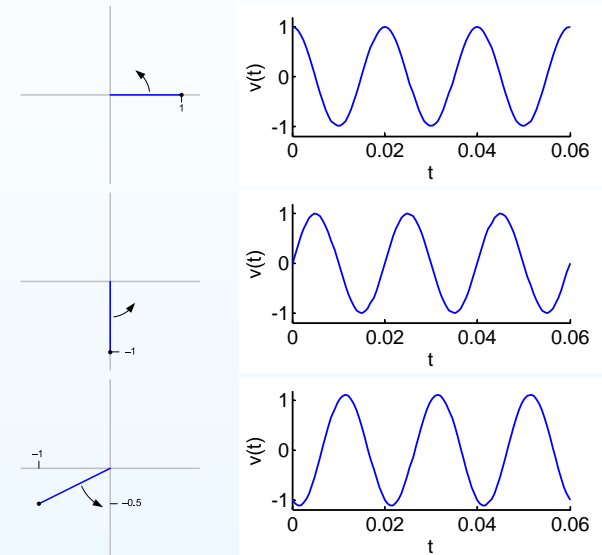

$$V = A \angle \phi = Ae^{j\phi}$$

$$v(t) = A \cos (2\pi ft + \phi)$$

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- **Phasor Examples**
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor Examples

$$V = 1, f = 50 \text{ Hz}$$

$$v(t) = \cos 2\pi ft$$

$$V = -j$$

$$v(t) = \sin 2\pi ft$$


$$V = -1 - 0.5j = 1.12 \angle -153^\circ$$

$$v(t) = -\cos 2\pi ft + 0.5 \sin 2\pi ft \\ = 1.12 \cos (2\pi ft - 2.68)$$

$$V = X + jY$$

$$v(t) = X \cos 2\pi ft - Y \sin 2\pi ft$$

Beware minus sign.

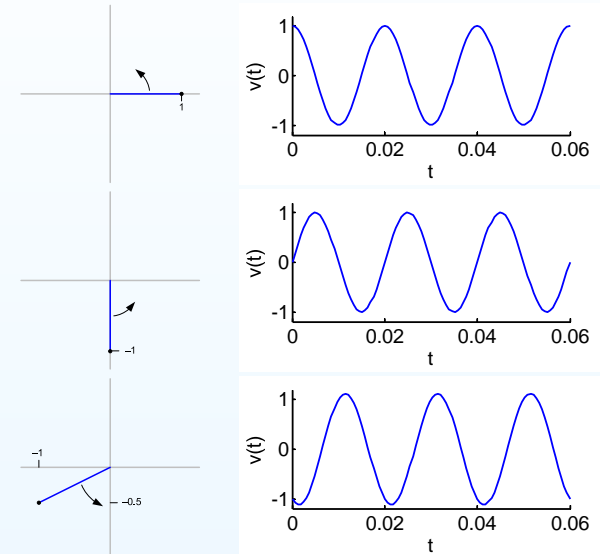

$$V = A \angle \phi = Ae^{j\phi}$$

$$v(t) = A \cos (2\pi ft + \phi)$$

A phasor represents an entire waveform (encompassing all time) as a single complex number. We assume the frequency, f , is known.

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- **Phasor Examples**
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor Examples

$$V = 1, f = 50 \text{ Hz}$$

$$v(t) = \cos 2\pi ft$$

$$V = -j$$

$$v(t) = \sin 2\pi ft$$


$$V = -1 - 0.5j = 1.12 \angle -153^\circ$$

$$v(t) = -\cos 2\pi ft + 0.5 \sin 2\pi ft \\ = 1.12 \cos (2\pi ft - 2.68)$$

$$V = X + jY$$

$$v(t) = X \cos 2\pi ft - Y \sin 2\pi ft$$

Beware minus sign.

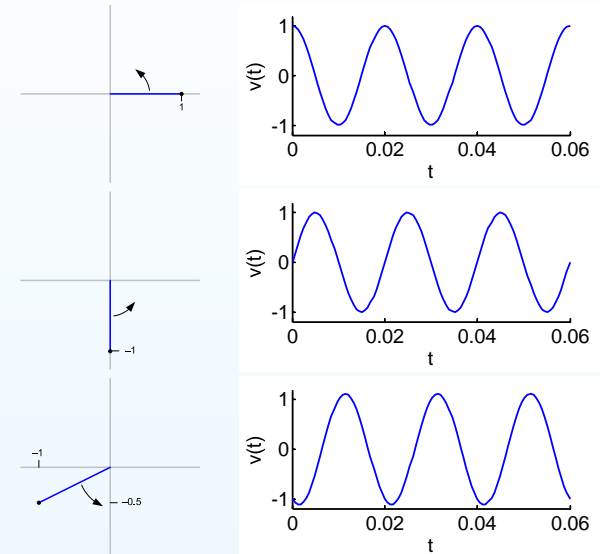

$$V = A \angle \phi = Ae^{j\phi}$$

$$v(t) = A \cos (2\pi ft + \phi)$$

A phasor represents an entire waveform (encompassing all time) as a single complex number. We assume the frequency, f , is known.

A phasor is not time-varying, so we use a capital letter: V .

A waveform is time-varying, so we use a small letter: $v(t)$.

Phasor Examples

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- **Phasor Examples**
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

$$V = 1, f = 50 \text{ Hz}$$

$$v(t) = \cos 2\pi ft$$

$$V = -j$$

$$v(t) = \sin 2\pi ft$$


$$V = -1 - 0.5j = 1.12 \angle -153^\circ$$

$$v(t) = -\cos 2\pi ft + 0.5 \sin 2\pi ft \\ = 1.12 \cos (2\pi ft - 2.68)$$

$$V = X + jY$$

$$v(t) = X \cos 2\pi ft - Y \sin 2\pi ft$$

Beware minus sign.

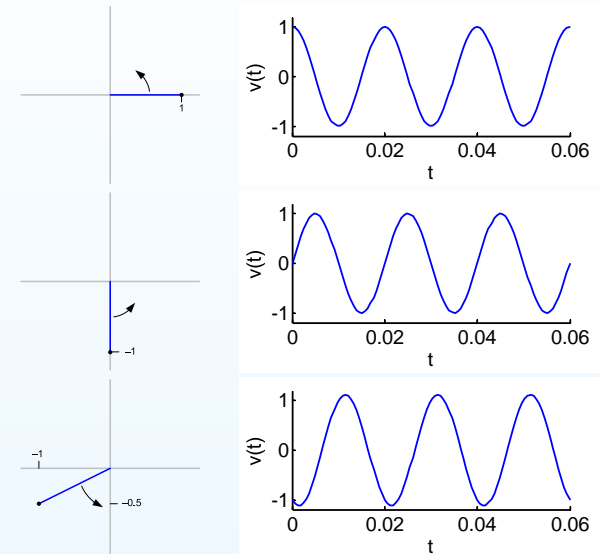

$$V = A \angle \phi = Ae^{j\phi}$$

$$v(t) = A \cos (2\pi ft + \phi)$$

A phasor represents an entire waveform (encompassing all time) as a single complex number. We assume the frequency, f , is known.

A phasor is not time-varying, so we use a capital letter: V .

A waveform is time-varying, so we use a small letter: $v(t)$.

Casio: $\text{Pol}(X, Y) \rightarrow A, \phi, \text{Rec}(A, \phi) \rightarrow X, Y$. Saved $\rightarrow X$ & Y mems.

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- **Phasor arithmetic**
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor arithmetic

Phasors

$$V = X + jY$$

Waveforms

$$v(t) = X \cos \omega t - Y \sin \omega t$$

where $\omega = 2\pi f$.

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- **Phasor arithmetic**
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor arithmetic

Phasors

$$V = X + jY$$

Waveforms

$$v(t) = X \cos \omega t - Y \sin \omega t$$

where $\omega = 2\pi f$.

$$a \times v(t)$$

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- **Phasor arithmetic**
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor arithmetic

Phasors

$$V = X + jY$$

Waveforms

$$v(t) = X \cos \omega t - Y \sin \omega t$$

where $\omega = 2\pi f$.

$$a \times v(t) = aX \cos \omega t - aY \sin \omega t$$

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- **Phasor arithmetic**
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor arithmetic

Phasors

$$V = X + jY$$

$$aV$$

Waveforms

$$v(t) = X \cos \omega t - Y \sin \omega t$$

where $\omega = 2\pi f$.

$$a \times v(t) = aX \cos \omega t - aY \sin \omega t$$

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- **Phasor arithmetic**
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor arithmetic

Phasors

$$V = X + jY$$

$$aV$$

Waveforms

$$v(t) = X \cos \omega t - Y \sin \omega t$$

where $\omega = 2\pi f$.

$$a \times v(t) = aX \cos \omega t - aY \sin \omega t$$

$$v_1(t) + v_2(t)$$

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- **Phasor arithmetic**
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor arithmetic

Phasors

$$V = X + jY$$

$$aV$$

$$V_1 + V_2$$

Waveforms

$$v(t) = X \cos \omega t - Y \sin \omega t$$

where $\omega = 2\pi f$.

$$a \times v(t) = aX \cos \omega t - aY \sin \omega t$$

$$v_1(t) + v_2(t)$$

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- **Phasor arithmetic**
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor arithmetic

Phasors

$$V = X + jY$$

$$aV$$

$$V_1 + V_2$$

Waveforms

$$v(t) = X \cos \omega t - Y \sin \omega t$$

where $\omega = 2\pi f$.

$$a \times v(t) = aX \cos \omega t - aY \sin \omega t$$

$$v_1(t) + v_2(t)$$

Adding or scaling is the same for waveforms and phasors.

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- **Phasor arithmetic**
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor arithmetic

Phasors

$$V = X + jY$$

$$aV$$

$$V_1 + V_2$$

Waveforms

$$v(t) = X \cos \omega t - Y \sin \omega t$$

where $\omega = 2\pi f$.

$$a \times v(t) = aX \cos \omega t - aY \sin \omega t$$

$$v_1(t) + v_2(t)$$

Adding or scaling is the same for waveforms and phasors.

$$\frac{dv}{dt} = -\omega X \sin \omega t - \omega Y \cos \omega t$$

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- **Phasor arithmetic**
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor arithmetic

Phasors

$$V = X + jY$$

$$aV$$

$$V_1 + V_2$$

Waveforms

$$v(t) = X \cos \omega t - Y \sin \omega t$$

$$\text{where } \omega = 2\pi f.$$

$$a \times v(t) = aX \cos \omega t - aY \sin \omega t$$

$$v_1(t) + v_2(t)$$

Adding or scaling is the same for waveforms and phasors.

$$\begin{aligned} \frac{dv}{dt} &= -\omega X \sin \omega t - \omega Y \cos \omega t \\ &= (-\omega Y) \cos \omega t - (\omega X) \sin \omega t \end{aligned}$$

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- **Phasor arithmetic**
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor arithmetic

Phasors

$$V = X + jY$$

$$aV$$

$$V_1 + V_2$$

Adding or scaling is the same for waveforms and phasors.

$$\dot{V} = (-\omega Y) + j(\omega X)$$

Waveforms

$$v(t) = X \cos \omega t - Y \sin \omega t$$

where $\omega = 2\pi f$.

$$a \times v(t) = aX \cos \omega t - aY \sin \omega t$$

$$v_1(t) + v_2(t)$$

$$\begin{aligned} \frac{dv}{dt} &= -\omega X \sin \omega t - \omega Y \cos \omega t \\ &= (-\omega Y) \cos \omega t - (\omega X) \sin \omega t \end{aligned}$$

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- **Phasor arithmetic**
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor arithmetic

Phasors

$$V = X + jY$$

$$aV$$

$$V_1 + V_2$$

Adding or scaling is the same for waveforms and phasors.

$$\begin{aligned}\dot{V} &= (-\omega Y) + j(\omega X) \\ &= j\omega(X + jY)\end{aligned}$$

Waveforms

$$v(t) = X \cos \omega t - Y \sin \omega t$$

where $\omega = 2\pi f$.

$$a \times v(t) = aX \cos \omega t - aY \sin \omega t$$

$$v_1(t) + v_2(t)$$

$$\begin{aligned}\frac{dv}{dt} &= -\omega X \sin \omega t - \omega Y \cos \omega t \\ &= (-\omega Y) \cos \omega t - (\omega X) \sin \omega t\end{aligned}$$

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- **Phasor arithmetic**
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor arithmetic

Phasors

$$V = X + jY$$

$$aV$$

$$V_1 + V_2$$

Adding or scaling is the same for waveforms and phasors.

$$\begin{aligned}\dot{V} &= (-\omega Y) + j(\omega X) \\ &= j\omega(X + jY) \\ &= j\omega V\end{aligned}$$

Waveforms

$$v(t) = X \cos \omega t - Y \sin \omega t$$

where $\omega = 2\pi f$.

$$a \times v(t) = aX \cos \omega t - aY \sin \omega t$$

$$v_1(t) + v_2(t)$$

$$\begin{aligned}\frac{dv}{dt} &= -\omega X \sin \omega t - \omega Y \cos \omega t \\ &= (-\omega Y) \cos \omega t - (\omega X) \sin \omega t\end{aligned}$$

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- **Phasor arithmetic**
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor arithmetic

Phasors

$$V = X + jY$$

$$aV$$

$$V_1 + V_2$$

Waveforms

$$v(t) = X \cos \omega t - Y \sin \omega t$$

$$\text{where } \omega = 2\pi f.$$

$$a \times v(t) = aX \cos \omega t - aY \sin \omega t$$

$$v_1(t) + v_2(t)$$

Adding or scaling is the same for waveforms and phasors.

$$\begin{aligned}\dot{V} &= (-\omega Y) + j(\omega X) \\ &= j\omega(X + jY) \\ &= j\omega V\end{aligned}$$

$$\begin{aligned}\frac{dv}{dt} &= -\omega X \sin \omega t - \omega Y \cos \omega t \\ &= (-\omega Y) \cos \omega t - (\omega X) \sin \omega t\end{aligned}$$

Differentiating waveforms corresponds to multiplying phasors by $j\omega$.

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- **Phasor arithmetic**
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor arithmetic

Phasors

$$V = X + jY$$

$$aV$$

$$V_1 + V_2$$

Waveforms

$$v(t) = X \cos \omega t - Y \sin \omega t$$

$$\text{where } \omega = 2\pi f.$$

$$a \times v(t) = aX \cos \omega t - aY \sin \omega t$$


$$v_1(t) + v_2(t)$$

Adding or scaling is the same for waveforms and phasors.

$$\begin{aligned}\dot{V} &= (-\omega Y) + j(\omega X) \\ &= j\omega(X + jY) \\ &= j\omega V\end{aligned}$$

$$\begin{aligned}\frac{dv}{dt} &= -\omega X \sin \omega t - \omega Y \cos \omega t \\ &= (-\omega Y) \cos \omega t - (\omega X) \sin \omega t\end{aligned}$$

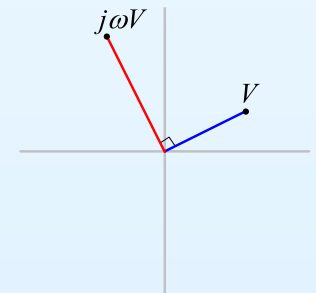Differentiating waveforms corresponds to multiplying phasors by $j\omega$.



10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- **Phasor arithmetic**
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Phasor arithmetic

Phasors

$$V = X + jY$$

$$aV$$

$$V_1 + V_2$$

Waveforms

$$v(t) = X \cos \omega t - Y \sin \omega t$$

where $\omega = 2\pi f$.

$$a \times v(t) = aX \cos \omega t - aY \sin \omega t$$

$$v_1(t) + v_2(t)$$


Adding or scaling is the same for waveforms and phasors.

$$\begin{aligned}\dot{V} &= (-\omega Y) + j(\omega X) \\ &= j\omega(X + jY) \\ &= j\omega V\end{aligned}$$

$$\begin{aligned}\frac{dv}{dt} &= -\omega X \sin \omega t - \omega Y \cos \omega t \\ &= (-\omega Y) \cos \omega t - (\omega X) \sin \omega t\end{aligned}$$

Differentiating waveforms corresponds to multiplying phasors by $j\omega$.

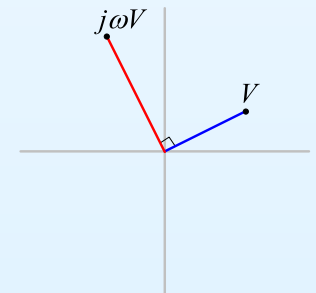Rotate anti-clockwise 90° and scale by $\omega = 2\pi f$.




Complex Impedances

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- **Complex Impedances**
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Resistor:

$$v(t) = Ri(t)$$

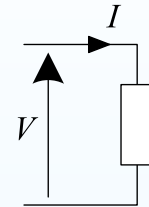


Complex Impedances

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- **Complex Impedances**
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Resistor:

$$v(t) = Ri(t) \Rightarrow V = RI$$

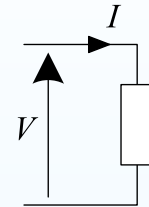


Complex Impedances

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- **Complex Impedances**
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Resistor:
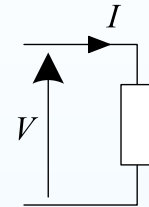
$$v(t) = Ri(t) \Rightarrow V = RI \Rightarrow \frac{V}{I} = R$$




Complex Impedances

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- **Complex Impedances**
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)


Resistor:
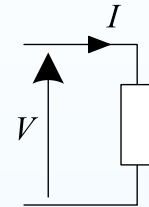
$$v(t) = Ri(t) \Rightarrow V = RI \Rightarrow \frac{V}{I} = R$$



Inductor:

$$v(t) = L \frac{di}{dt}$$

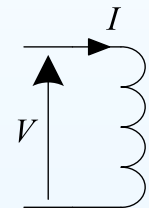


Complex Impedances

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- **Complex Impedances**
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)


Resistor:
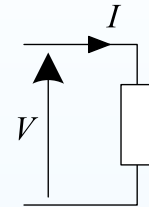
$$v(t) = Ri(t) \Rightarrow V = RI \Rightarrow \frac{V}{I} = R$$



Inductor:
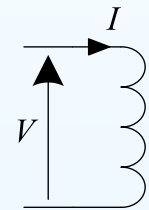
$$v(t) = L \frac{di}{dt} \Rightarrow V = j\omega LI$$




Complex Impedances

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- **Complex Impedances**
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)


Resistor:
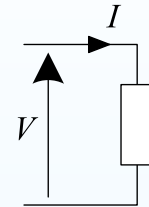
$$v(t) = Ri(t) \Rightarrow V = RI \Rightarrow \frac{V}{I} = R$$



Inductor:
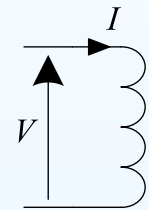
$$v(t) = L \frac{di}{dt} \Rightarrow V = j\omega LI \Rightarrow \frac{V}{I} = j\omega L$$




Complex Impedances

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- **Complex Impedances**
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)


Resistor:
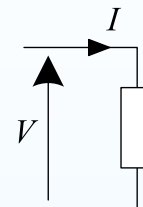
$$v(t) = Ri(t) \Rightarrow V = RI \Rightarrow \frac{V}{I} = R$$




Inductor:
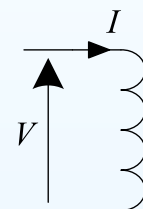
$$v(t) = L \frac{di}{dt} \Rightarrow V = j\omega LI \Rightarrow \frac{V}{I} = j\omega L$$



Capacitor:

$$i(t) = C \frac{dv}{dt}$$

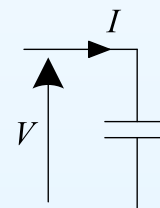


Complex Impedances

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- **Complex Impedances**
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)


Resistor:
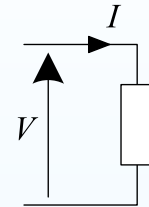
$$v(t) = Ri(t) \Rightarrow V = RI \Rightarrow \frac{V}{I} = R$$




Inductor:
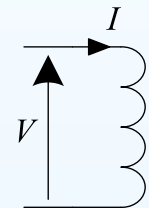
$$v(t) = L \frac{di}{dt} \Rightarrow V = j\omega LI \Rightarrow \frac{V}{I} = j\omega L$$



Capacitor:
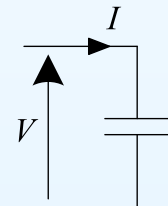
$$i(t) = C \frac{dv}{dt} \Rightarrow I = j\omega CV$$




Complex Impedances

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- **Complex Impedances**
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)


Resistor:
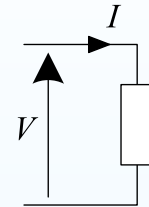
$$v(t) = Ri(t) \Rightarrow V = RI \Rightarrow \frac{V}{I} = R$$




Inductor:
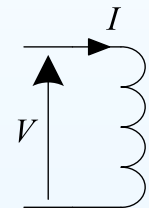
$$v(t) = L \frac{di}{dt} \Rightarrow V = j\omega LI \Rightarrow \frac{V}{I} = j\omega L$$



Capacitor:
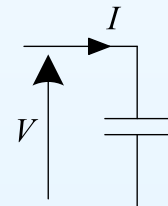
$$i(t) = C \frac{dv}{dt} \Rightarrow I = j\omega CV \Rightarrow \frac{V}{I} = \frac{1}{j\omega C}$$




Complex Impedances

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- **Complex Impedances**
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)


Resistor:
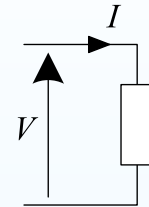
$$v(t) = Ri(t) \Rightarrow V = RI \Rightarrow \frac{V}{I} = R$$




Inductor:
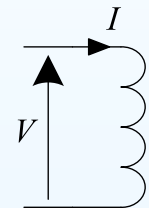
$$v(t) = L \frac{di}{dt} \Rightarrow V = j\omega LI \Rightarrow \frac{V}{I} = j\omega L$$



Capacitor:
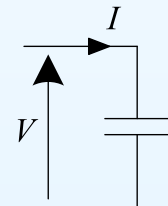
$$i(t) = C \frac{dv}{dt} \Rightarrow I = j\omega CV \Rightarrow \frac{V}{I} = \frac{1}{j\omega C}$$



For all three components, phasors obey Ohm's law if we use the **complex impedances** $j\omega L$ and $\frac{1}{j\omega C}$ as the “resistance” of an inductor or capacitor.


Complex Impedances

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- **Complex Impedances**
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)


Resistor:
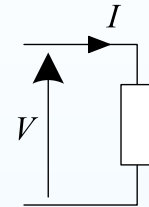
$$v(t) = Ri(t) \Rightarrow V = RI \Rightarrow \frac{V}{I} = R$$




Inductor:
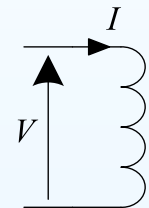
$$v(t) = L \frac{di}{dt} \Rightarrow V = j\omega LI \Rightarrow \frac{V}{I} = j\omega L$$



Capacitor:
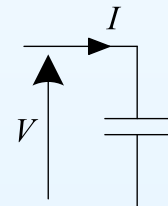
$$i(t) = C \frac{dv}{dt} \Rightarrow I = j\omega CV \Rightarrow \frac{V}{I} = \frac{1}{j\omega C}$$



For all three components, phasors obey Ohm's law if we use the **complex impedances** $j\omega L$ and $\frac{1}{j\omega C}$ as the “resistance” of an inductor or capacitor.



If all sources in a circuit are sine waves having the same frequency, we can do circuit analysis exactly as before by using complex impedances.

Phasor Analysis

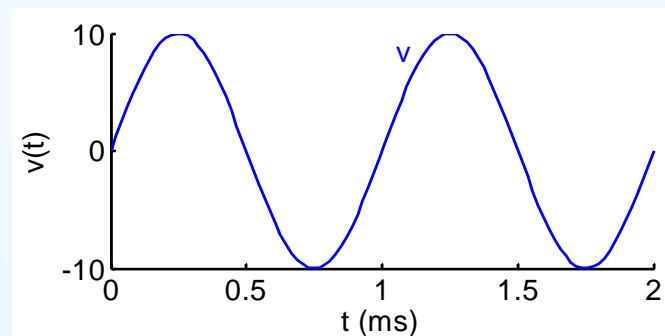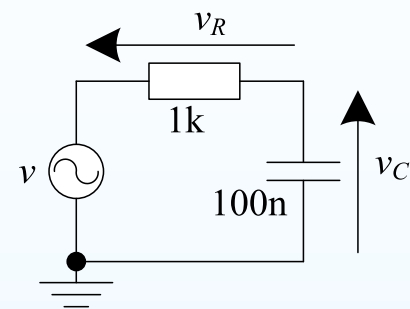10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- **Phasor Analysis**
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Given $v = 10 \sin \omega t$ where $\omega = 2\pi \times 1000$, find $v_C(t)$.



Phasor Analysis



10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- **Phasor Analysis**
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Given $v = 10 \sin \omega t$ where $\omega = 2\pi \times 1000$, find $v_C(t)$.

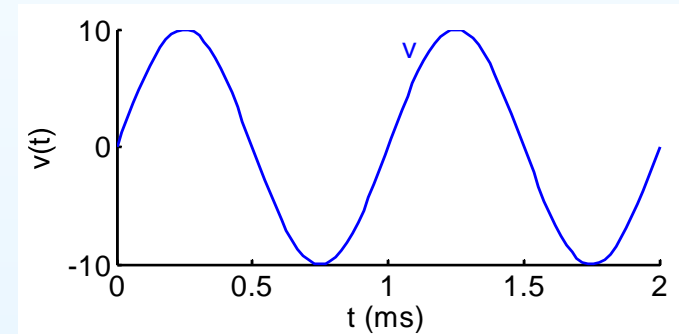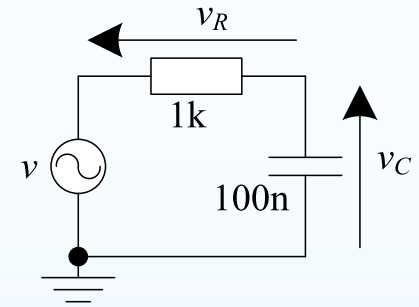(1) Find capacitor complex impedance

$$Z = \frac{1}{j\omega C} = \frac{1}{6.28j \times 10^{-4}} = -1592j$$



Phasor Analysis

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- **Phasor Analysis**
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)



Given $v = 10 \sin \omega t$ where $\omega = 2\pi \times 1000$, find $v_C(t)$.

(1) Find capacitor complex impedance

$$Z = \frac{1}{j\omega C} = \frac{1}{6.28j \times 10^{-4}} = -1592j$$

(2) Solve circuit with phasors

$$V_C = V \times \frac{Z}{R+Z}$$

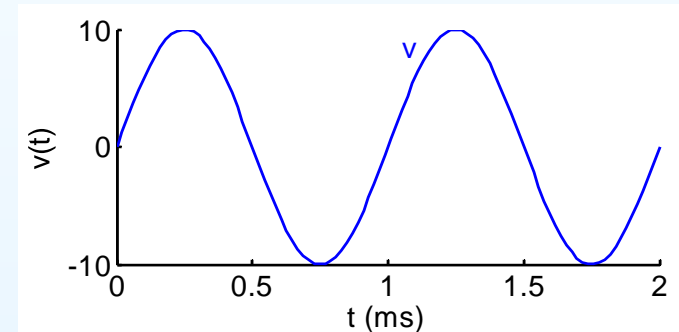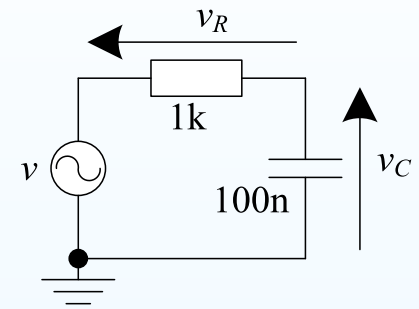

Phasor Analysis

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- **Phasor Analysis**
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)



Given $v = 10 \sin \omega t$ where $\omega = 2\pi \times 1000$, find $v_C(t)$.

(1) Find capacitor complex impedance

$$Z = \frac{1}{j\omega C} = \frac{1}{6.28j \times 10^{-4}} = -1592j$$

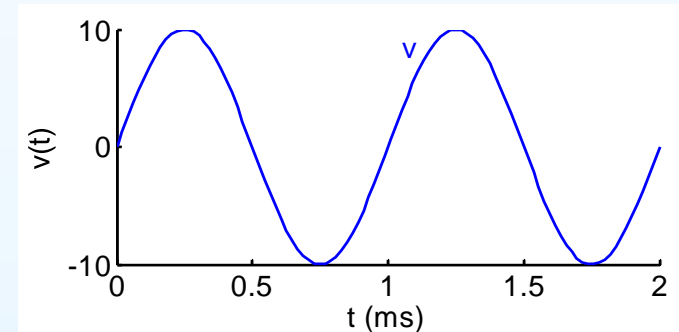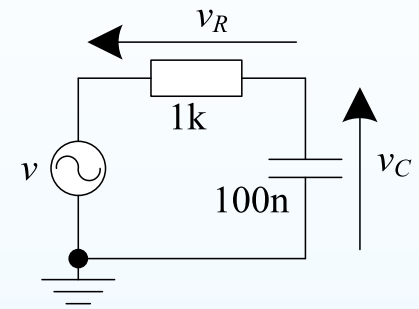(2) Solve circuit with phasors

$$\begin{aligned} V_C &= V \times \frac{Z}{R+Z} \\ &= -10j \times \frac{-1592j}{1000 - 1592j} \end{aligned}$$



Phasor Analysis

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- **Phasor Analysis**
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)



Given $v = 10 \sin \omega t$ where $\omega = 2\pi \times 1000$, find $v_C(t)$.

(1) Find capacitor complex impedance

$$Z = \frac{1}{j\omega C} = \frac{1}{6.28j \times 10^{-4}} = -1592j$$

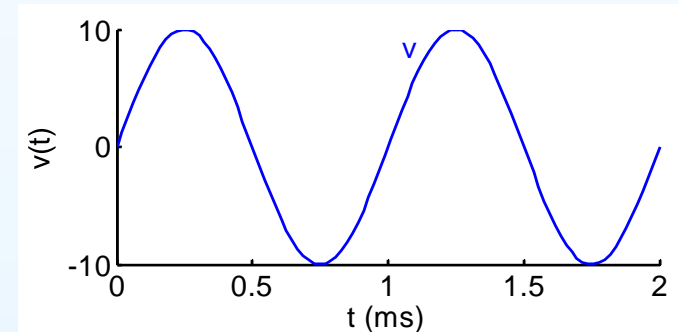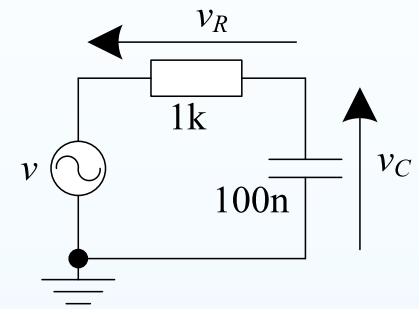(2) Solve circuit with phasors

$$\begin{aligned} V_C &= V \times \frac{Z}{R+Z} \\ &= -10j \times \frac{-1592j}{1000 - 1592j} \\ &= -4.5 - 7.2j = 8.47 \angle -122^\circ \end{aligned}$$



Phasor Analysis

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- **Phasor Analysis**
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)



Given $v = 10 \sin \omega t$ where $\omega = 2\pi \times 1000$, find $v_C(t)$.

(1) Find capacitor complex impedance

$$Z = \frac{1}{j\omega C} = \frac{1}{6.28j \times 10^{-4}} = -1592j$$

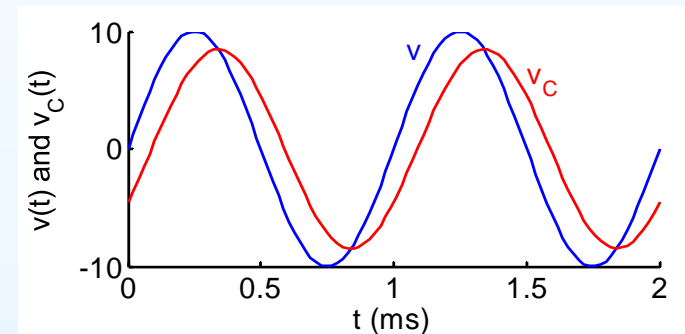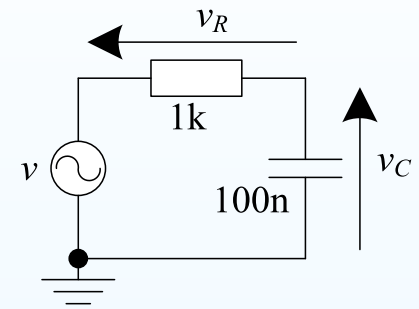(2) Solve circuit with phasors

$$\begin{aligned} V_C &= V \times \frac{Z}{R+Z} \\ &= -10j \times \frac{-1592j}{1000 - 1592j} \\ &= -4.5 - 7.2j = 8.47 \angle -122^\circ \\ v_C &= 8.47 \cos(\omega t - 122^\circ) \end{aligned}$$



Phasor Analysis

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- **Phasor Analysis**
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Given $v = 10 \sin \omega t$ where $\omega = 2\pi \times 1000$, find $v_C(t)$.

(1) Find capacitor complex impedance

$$Z = \frac{1}{j\omega C} = \frac{1}{6.28j \times 10^{-4}} = -1592j$$

(2) Solve circuit with phasors



$$\begin{aligned} V_C &= V \times \frac{Z}{R+Z} \\ &= -10j \times \frac{-1592j}{1000 - 1592j} \\ &= -4.5 - 7.2j = 8.47 \angle -122^\circ \\ v_C &= 8.47 \cos(\omega t - 122^\circ) \end{aligned}$$

(3) Draw a *phasor diagram*:

$$V = -10j$$

$$V_C = -4.5 - 7.2j$$
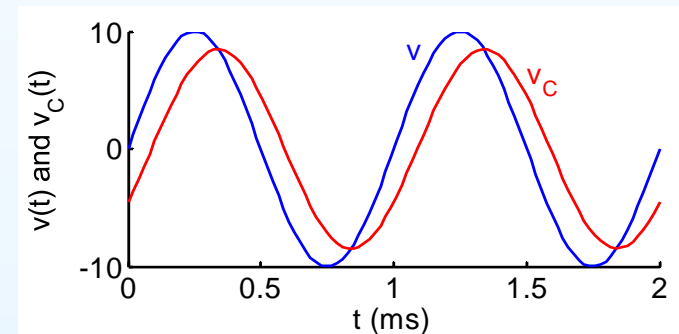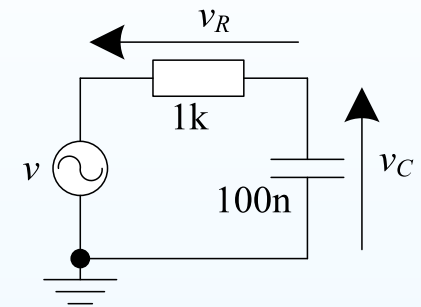
$$V_R = V - V_C = 4.5 - 2.8j = 5.3 \angle -32^\circ$$



Phasor Analysis

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- **Phasor Analysis**
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Given $v = 10 \sin \omega t$ where $\omega = 2\pi \times 1000$, find $v_C(t)$.

(1) Find capacitor complex impedance

$$Z = \frac{1}{j\omega C} = \frac{1}{6.28j \times 10^{-4}} = -1592j$$

(2) Solve circuit with phasors




$$\begin{aligned} V_C &= V \times \frac{Z}{R+Z} \\ &= -10j \times \frac{-1592j}{1000 - 1592j} \\ &= -4.5 - 7.2j = 8.47 \angle -122^\circ \\ v_C &= 8.47 \cos(\omega t - 122^\circ) \end{aligned}$$

(3) Draw a *phasor diagram*:

$$V = -10j$$

$$V_C = -4.5 - 7.2j$$
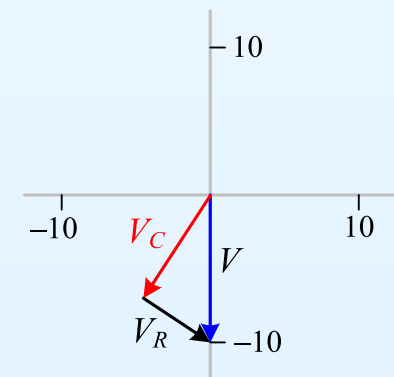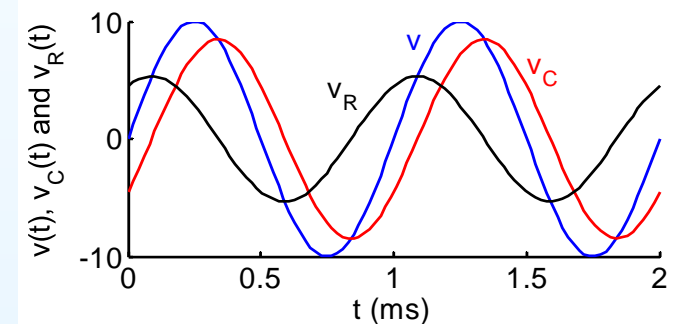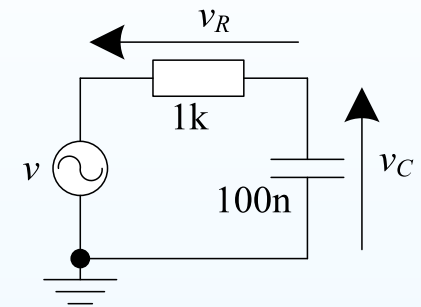
$$V_R = V - V_C = 4.5 - 2.8j = 5.3 \angle -32^\circ$$



Phasor Analysis

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- **Phasor Analysis**
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Given $v = 10 \sin \omega t$ where $\omega = 2\pi \times 1000$, find $v_C(t)$.

(1) Find capacitor complex impedance

$$Z = \frac{1}{j\omega C} = \frac{1}{6.28j \times 10^{-4}} = -1592j$$

(2) Solve circuit with phasors

$$\begin{aligned} V_C &= V \times \frac{Z}{R+Z} \\ &= -10j \times \frac{-1592j}{1000-1592j} \\ &= -4.5 - 7.2j = 8.47 \angle -122^\circ \\ v_C &= 8.47 \cos(\omega t - 122^\circ) \end{aligned}$$




(3) Draw a *phasor diagram*:

$$V = -10j$$

$$V_C = -4.5 - 7.2j$$

$$V_R = V - V_C = 4.5 - 2.8j = 5.3 \angle -32^\circ$$

Phasors add like vectors

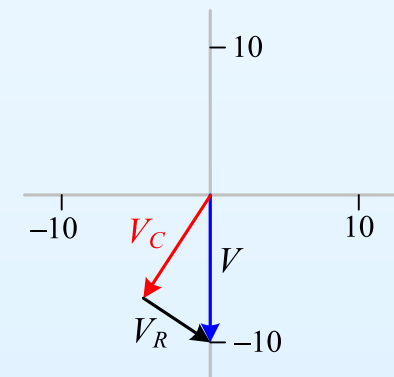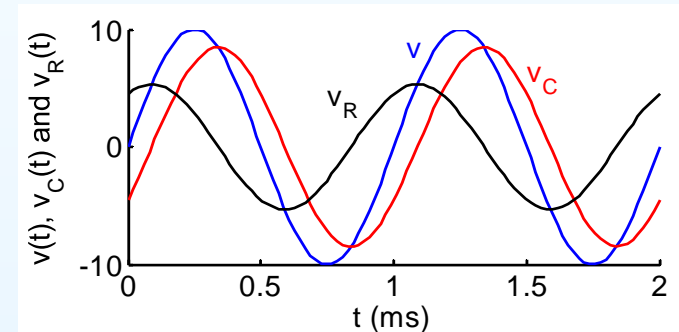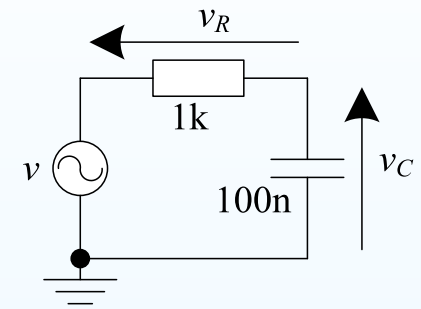

CIVIL

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Capacitors: $i = C \frac{dv}{dt} \Rightarrow I \text{ leads } V$

Inductors: $v = L \frac{di}{dt} \Rightarrow V \text{ leads } I$

CIVIL

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- **CIVIL**
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Capacitors: $i = C \frac{dv}{dt} \Rightarrow I \text{ leads } V$

Inductors: $v = L \frac{di}{dt} \Rightarrow V \text{ leads } I$

Mnemonic: **CIVIL** = “In a capacitor I lead V but V leads I in an inductor”.

CIVIL

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Capacitors: $i = C \frac{dv}{dt} \Rightarrow I \text{ leads } V$

Inductors: $v = L \frac{di}{dt} \Rightarrow V \text{ leads } I$

Mnemonic: **CIVIL** = “In a capacitor I lead V but V leads I in an inductor”.

COMPLEX ARITHMETIC TRICKS:

CIVIL

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- **CIVIL**
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Capacitors: $i = C \frac{dv}{dt} \Rightarrow I \text{ leads } V$

Inductors: $v = L \frac{di}{dt} \Rightarrow V \text{ leads } I$

Mnemonic: **CIVIL** = “In a capacitor I lead V but V leads I in an inductor”.

COMPLEX ARITHMETIC TRICKS:

$$(1) j \times j = -j \times -j = -1$$

CIVIL

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- **CIVIL**
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Capacitors: $i = C \frac{dv}{dt} \Rightarrow I \text{ leads } V$

Inductors: $v = L \frac{di}{dt} \Rightarrow V \text{ leads } I$

Mnemonic: **CIVIL** = “In a capacitor I lead V but V leads I in an inductor”.

COMPLEX ARITHMETIC TRICKS:

$$(1) j \times j = -j \times -j = -1$$

$$(2) \frac{1}{j} = -j$$

CIVIL

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- **CIVIL**
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Capacitors: $i = C \frac{dv}{dt} \Rightarrow I \text{ leads } V$

Inductors: $v = L \frac{di}{dt} \Rightarrow V \text{ leads } I$

Mnemonic: **CIVIL** = “In a capacitor I lead V but V leads I in an inductor”.

COMPLEX ARITHMETIC TRICKS:

$$(1) j \times j = -j \times -j = -1$$

$$(2) \frac{1}{j} = -j$$

$$(3) a + jb = r\angle\theta = re^{j\theta} \text{ where } r = \sqrt{a^2 + b^2} \text{ and } \theta = \arctan \frac{b}{a} \\ (\pm 180^\circ \text{ if } a < 0)$$

CIVIL

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- **CIVIL**
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Capacitors: $i = C \frac{dv}{dt} \Rightarrow I \text{ leads } V$

Inductors: $v = L \frac{di}{dt} \Rightarrow V \text{ leads } I$

Mnemonic: **CIVIL** = "In a capacitor I lead V but V leads I in an inductor".

COMPLEX ARITHMETIC TRICKS:

$$(1) j \times j = -j \times -j = -1$$

$$(2) \frac{1}{j} = -j$$

$$(3) a + jb = r\angle\theta = re^{j\theta} \text{ where } r = \sqrt{a^2 + b^2} \text{ and } \theta = \arctan \frac{b}{a} \\ (\pm 180^\circ \text{ if } a < 0)$$

$$(4) r\angle\theta = re^{j\theta} = (r \cos \theta) + j (r \sin \theta)$$

CIVIL

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Capacitors: $i = C \frac{dv}{dt} \Rightarrow I \text{ leads } V$

Inductors: $v = L \frac{di}{dt} \Rightarrow V \text{ leads } I$

Mnemonic: **CIVIL** = “In a capacitor I lead V but V leads I in an inductor”.

COMPLEX ARITHMETIC TRICKS:

$$(1) j \times j = -j \times -j = -1$$

$$(2) \frac{1}{j} = -j$$

$$(3) a + jb = r \angle \theta = re^{j\theta} \text{ where } r = \sqrt{a^2 + b^2} \text{ and } \theta = \arctan \frac{b}{a} \\ (\pm 180^\circ \text{ if } a < 0)$$

$$(4) r \angle \theta = re^{j\theta} = (r \cos \theta) + j (r \sin \theta)$$

$$(5) a \angle \theta \times b \angle \phi = ab \angle (\theta + \phi) \text{ and } \frac{a \angle \theta}{b \angle \phi} = \frac{a}{b} \angle (\theta - \phi).$$

Multiplication and division are much easier in polar form.

CIVIL

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- **CIVIL**
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Capacitors: $i = C \frac{dv}{dt} \Rightarrow I \text{ leads } V$

Inductors: $v = L \frac{di}{dt} \Rightarrow V \text{ leads } I$

Mnemonic: **CIVIL** = "In a capacitor I lead V but V leads I in an inductor".

COMPLEX ARITHMETIC TRICKS:

$$(1) j \times j = -j \times -j = -1$$

$$(2) \frac{1}{j} = -j$$

$$(3) a + jb = r \angle \theta = re^{j\theta} \text{ where } r = \sqrt{a^2 + b^2} \text{ and } \theta = \arctan \frac{b}{a} \\ (\pm 180^\circ \text{ if } a < 0)$$

$$(4) r \angle \theta = re^{j\theta} = (r \cos \theta) + j (r \sin \theta)$$

$$(5) a \angle \theta \times b \angle \phi = ab \angle (\theta + \phi) \text{ and } \frac{a \angle \theta}{b \angle \phi} = \frac{a}{b} \angle (\theta - \phi).$$

Multiplication and division are much easier in polar form.

(6) **All scientific calculators** will convert rectangular to/from polar form.

CIVIL

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- **CIVIL**
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Capacitors: $i = C \frac{dv}{dt} \Rightarrow I \text{ leads } V$

Inductors: $v = L \frac{di}{dt} \Rightarrow V \text{ leads } I$

Mnemonic: **CIVIL** = “In a capacitor I lead V but V leads I in an inductor”.

COMPLEX ARITHMETIC TRICKS:

$$(1) j \times j = -j \times -j = -1$$

$$(2) \frac{1}{j} = -j$$

$$(3) a + jb = r \angle \theta = re^{j\theta} \text{ where } r = \sqrt{a^2 + b^2} \text{ and } \theta = \arctan \frac{b}{a} (\pm 180^\circ \text{ if } a < 0)$$

$$(4) r \angle \theta = re^{j\theta} = (r \cos \theta) + j (r \sin \theta)$$

$$(5) a \angle \theta \times b \angle \phi = ab \angle (\theta + \phi) \text{ and } \frac{a \angle \theta}{b \angle \phi} = \frac{a}{b} \angle (\theta - \phi).$$

Multiplication and division are much easier in polar form.

(6) **All scientific calculators** will convert rectangular to/from polar form.

Casio fx-991 (available in all exams except Maths) will do complex arithmetic $(+, -, \times, \div, x^2, \frac{1}{x}, |x|, x^*)$ in CMPLX mode.

Learn how to use this: it will save lots of time and errors.

Impedance and Admittance

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- **Impedance and Admittance**
- Summary (Irwin/Nelms Ch 8)

For any network (resistors+capacitors+inductors):

Impedance and Admittance

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- **Impedance and Admittance**
- Summary (Irwin/Nelms Ch 8)

For any network (resistors+capacitors+inductors):

(1) **Impedance** = **Resistance** + $j \times$ **Reactance**

$$Z = R + jX (\Omega)$$

Impedance and Admittance

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- **Impedance and Admittance**
- Summary (Irwin/Nelms Ch 8)

For any network (resistors+capacitors+inductors):

(1) **Impedance** = **Resistance** + $j \times$ **Reactance**

$$Z = R + jX (\Omega)$$

$$|Z|^2 = R^2 + X^2$$

$$\angle Z = \arctan \frac{X}{R}$$

Impedance and Admittance

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- **Impedance and Admittance**
- Summary (Irwin/Nelms Ch 8)

For any network (resistors+capacitors+inductors):

(1) **Impedance** = **Resistance** + $j \times$ **Reactance**

$$Z = R + jX (\Omega)$$

$$|Z|^2 = R^2 + X^2$$

$$\angle Z = \arctan \frac{X}{R}$$

(2) **Admittance** = $\frac{1}{\text{Impedance}}$ = **Conductance** + $j \times$ **Susceptance**

$$Y = \frac{1}{Z} = G + jB (\text{S})$$

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Impedance and Admittance

For any network (resistors+capacitors+inductors):

(1) **Impedance** = **Resistance** + $j \times$ **Reactance**

$$Z = R + jX (\Omega)$$

$$|Z|^2 = R^2 + X^2$$

$$\angle Z = \arctan \frac{X}{R}$$

(2) **Admittance** = $\frac{1}{\text{Impedance}}$ = **Conductance** + $j \times$ **Susceptance**

$$Y = \frac{1}{Z} = G + jB (\text{S})$$

$$|Y|^2 = \frac{1}{|Z|^2} = G^2 + B^2$$

$$\angle Y = -\angle Z = \arctan \frac{B}{G}$$

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Impedance and Admittance

For any network (resistors+capacitors+inductors):

(1) **Impedance** = Resistance + $j \times$ Reactance

$$Z = R + jX (\Omega)$$

$$|Z|^2 = R^2 + X^2$$

$$\angle Z = \arctan \frac{X}{R}$$

(2) **Admittance** = $\frac{1}{\text{Impedance}}$ = Conductance + $j \times$ Susceptance

$$Y = \frac{1}{Z} = G + jB (\text{S})$$

$$|Y|^2 = \frac{1}{|Z|^2} = G^2 + B^2$$

$$\angle Y = -\angle Z = \arctan \frac{B}{G}$$

Note:

$$Y = G + jB = \frac{1}{Z}$$

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Impedance and Admittance

For any network (resistors+capacitors+inductors):

(1) **Impedance** = Resistance + $j \times$ Reactance

$$Z = R + jX (\Omega)$$

$$|Z|^2 = R^2 + X^2$$

$$\angle Z = \arctan \frac{X}{R}$$

(2) **Admittance** = $\frac{1}{\text{Impedance}}$ = Conductance + $j \times$ Susceptance

$$Y = \frac{1}{Z} = G + jB (\text{S})$$

$$|Y|^2 = \frac{1}{|Z|^2} = G^2 + B^2$$

$$\angle Y = -\angle Z = \arctan \frac{B}{G}$$

Note:

$$Y = G + jB = \frac{1}{Z} = \frac{1}{R + jX}$$

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Impedance and Admittance

For any network (resistors+capacitors+inductors):

(1) **Impedance** = Resistance + $j \times$ Reactance

$$Z = R + jX (\Omega)$$

$$|Z|^2 = R^2 + X^2$$

$$\angle Z = \arctan \frac{X}{R}$$

(2) **Admittance** = $\frac{1}{\text{Impedance}}$ = Conductance + $j \times$ Susceptance

$$Y = \frac{1}{Z} = G + jB (\text{S})$$

$$|Y|^2 = \frac{1}{|Z|^2} = G^2 + B^2$$

$$\angle Y = -\angle Z = \arctan \frac{B}{G}$$

Note:

$$Y = G + jB = \frac{1}{Z} = \frac{1}{R+jX} = \frac{R}{R^2+X^2} + j \frac{-X}{R^2+X^2}$$

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Impedance and Admittance

For any network (resistors+capacitors+inductors):

(1) **Impedance** = Resistance + $j \times$ Reactance

$$Z = R + jX (\Omega)$$

$$|Z|^2 = R^2 + X^2$$

$$\angle Z = \arctan \frac{X}{R}$$

(2) **Admittance** = $\frac{1}{\text{Impedance}}$ = Conductance + $j \times$ Susceptance

$$Y = \frac{1}{Z} = G + jB (\text{S})$$

$$|Y|^2 = \frac{1}{|Z|^2} = G^2 + B^2$$

$$\angle Y = -\angle Z = \arctan \frac{B}{G}$$

Note:

$$Y = G + jB = \frac{1}{Z} = \frac{1}{R + jX} = \frac{R}{R^2 + X^2} + j \frac{-X}{R^2 + X^2}$$

$$\text{So } G = \frac{R}{R^2 + X^2} \text{ and } B = \frac{-X}{R^2 + X^2}$$

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Impedance and Admittance

For any network (resistors+capacitors+inductors):

(1) **Impedance** = Resistance + $j \times$ Reactance

$$Z = R + jX (\Omega)$$

$$|Z|^2 = R^2 + X^2$$

$$\angle Z = \arctan \frac{X}{R}$$

(2) **Admittance** = $\frac{1}{\text{Impedance}}$ = Conductance + $j \times$ Susceptance

$$Y = \frac{1}{Z} = G + jB (\text{S})$$

$$|Y|^2 = \frac{1}{|Z|^2} = G^2 + B^2$$

$$\angle Y = -\angle Z = \arctan \frac{B}{G}$$

Note:

$$Y = G + jB = \frac{1}{Z} = \frac{1}{R + jX} = \frac{R}{R^2 + X^2} + j \frac{-X}{R^2 + X^2}$$

$$\text{So } G = \frac{R}{R^2 + X^2} \text{ and } B = \frac{-X}{R^2 + X^2}$$

Beware: $G \neq \frac{1}{R}$ unless $X = 0$.

Summary (Irwin/Nelms Ch 8)

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

- Sine waves are the only bounded signals whose shape is unchanged by differentiation.

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Summary (Irwin/Nelms Ch 8)

- Sine waves are the only bounded signals whose shape is unchanged by differentiation.
- Think of a sine wave as the projection of a rotating rod onto the horizontal (or real) axis.
 - A *phasor* is a complex number representing the length and position of the rod at time $t = 0$.

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Summary (Irwin/Nelms Ch 8)

- Sine waves are the only bounded signals whose shape is unchanged by differentiation.
- Think of a sine wave as the projection of a rotating rod onto the horizontal (or real) axis.
 - A *phasor* is a complex number representing the length and position of the rod at time $t = 0$.
 - If $V = a + jb = r\angle\theta = re^{j\theta}$, then
$$v(t) = a \cos \omega t - b \sin \omega t = r \cos(\omega t + \theta) = \Re(Ve^{j\omega t})$$

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Summary (Irwin/Nelms Ch 8)

- Sine waves are the only bounded signals whose shape is unchanged by differentiation.
- Think of a sine wave as the projection of a rotating rod onto the horizontal (or real) axis.
 - A *phasor* is a complex number representing the length and position of the rod at time $t = 0$.
 - If $V = a + jb = r\angle\theta = re^{j\theta}$, then
$$v(t) = a \cos \omega t - b \sin \omega t = r \cos(\omega t + \theta) = \Re(Ve^{j\omega t})$$
 - The *angular frequency* $\omega = 2\pi f$ is assumed known.

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- **Summary (Irwin/Nelms Ch 8)**

Summary (Irwin/Nelms Ch 8)

- Sine waves are the only bounded signals whose shape is unchanged by differentiation.
- Think of a sine wave as the projection of a rotating rod onto the horizontal (or real) axis.
 - A *phasor* is a complex number representing the length and position of the rod at time $t = 0$.
 - If $V = a + jb = r\angle\theta = re^{j\theta}$, then
$$v(t) = a \cos \omega t - b \sin \omega t = r \cos(\omega t + \theta) = \Re(Ve^{j\omega t})$$
 - The *angular frequency* $\omega = 2\pi f$ is assumed known.
- If **all sources in a linear circuit are sine waves having the same frequency**, we can use phasors for circuit analysis:

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Summary (Irwin/Nelms Ch 8)

- Sine waves are the only bounded signals whose shape is unchanged by differentiation.
- Think of a sine wave as the projection of a rotating rod onto the horizontal (or real) axis.
 - A *phasor* is a complex number representing the length and position of the rod at time $t = 0$.
 - If $V = a + jb = r\angle\theta = re^{j\theta}$, then
$$v(t) = a \cos \omega t - b \sin \omega t = r \cos(\omega t + \theta) = \Re(Ve^{j\omega t})$$
 - The *angular frequency* $\omega = 2\pi f$ is assumed known.
- If all sources in a linear circuit are sine waves having the same frequency, we can use phasors for circuit analysis:
 - Use complex impedances: $j\omega L$ and $\frac{1}{j\omega C}$

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- **Summary (Irwin/Nelms Ch 8)**

Summary (Irwin/Nelms Ch 8)

- Sine waves are the only bounded signals whose shape is unchanged by differentiation.
- Think of a sine wave as the projection of a rotating rod onto the horizontal (or real) axis.
 - A *phasor* is a complex number representing the length and position of the rod at time $t = 0$.
 - If $V = a + jb = r\angle\theta = re^{j\theta}$, then
$$v(t) = a \cos \omega t - b \sin \omega t = r \cos(\omega t + \theta) = \Re(Ve^{j\omega t})$$
 - The *angular frequency* $\omega = 2\pi f$ is assumed known.
- If **all sources in a linear circuit are sine waves having the same frequency**, we can use phasors for circuit analysis:
 - Use complex impedances: $j\omega L$ and $\frac{1}{j\omega C}$
 - Mnemonic: CIVIL tells you whether I leads V or vice versa (“leads” means “reaches its peak before”).

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

Summary (Irwin/Nelms Ch 8)

- Sine waves are the only bounded signals whose shape is unchanged by differentiation.
- Think of a sine wave as the projection of a rotating rod onto the horizontal (or real) axis.
 - A *phasor* is a complex number representing the length and position of the rod at time $t = 0$.
 - If $V = a + jb = r\angle\theta = re^{j\theta}$, then
$$v(t) = a \cos \omega t - b \sin \omega t = r \cos(\omega t + \theta) = \Re(Ve^{j\omega t})$$
 - The *angular frequency* $\omega = 2\pi f$ is assumed known.
- If **all sources in a linear circuit are sine waves having the same frequency**, we can use phasors for circuit analysis:
 - Use complex impedances: $j\omega L$ and $\frac{1}{j\omega C}$
 - Mnemonic: CIVIL tells you whether I leads V or vice versa (“leads” means “reaches its peak before”).
 - Phasors eliminate time from equations 😊

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- **Summary (Irwin/Nelms Ch 8)**

Summary (Irwin/Nelms Ch 8)

- Sine waves are the only bounded signals whose shape is unchanged by differentiation.
- Think of a sine wave as the projection of a rotating rod onto the horizontal (or real) axis.
 - A *phasor* is a complex number representing the length and position of the rod at time $t = 0$.
 - If $V = a + jb = r\angle\theta = re^{j\theta}$, then
$$v(t) = a \cos \omega t - b \sin \omega t = r \cos(\omega t + \theta) = \Re(Ve^{j\omega t})$$
 - The *angular frequency* $\omega = 2\pi f$ is assumed known.
- If **all sources in a linear circuit are sine waves having the same frequency**, we can use phasors for circuit analysis:
 - Use complex impedances: $j\omega L$ and $\frac{1}{j\omega C}$
 - Mnemonic: CIVIL tells you whether I leads V or vice versa (“leads” means “reaches its peak before”).
 - Phasors eliminate time from equations 😊, converts simultaneous **differential** equations into simultaneous **linear** equations 😊😊😊.

Summary (Irwin/Nelms Ch 8)

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

- Sine waves are the only bounded signals whose shape is unchanged by differentiation.
- Think of a sine wave as the projection of a rotating rod onto the horizontal (or real) axis.
 - A *phasor* is a complex number representing the length and position of the rod at time $t = 0$.
 - If $V = a + jb = r\angle\theta = re^{j\theta}$, then
$$v(t) = a \cos \omega t - b \sin \omega t = r \cos(\omega t + \theta) = \Re(Ve^{j\omega t})$$
 - The *angular frequency* $\omega = 2\pi f$ is assumed known.
- If **all sources in a linear circuit are sine waves having the same frequency**, we can use phasors for circuit analysis:
 - Use complex impedances: $j\omega L$ and $\frac{1}{j\omega C}$
 - Mnemonic: CIVIL tells you whether I leads V or vice versa (“leads” means “reaches its peak before”).
 - Phasors eliminate time from equations 😊, converts simultaneous **differential** equations into simultaneous **linear** equations 😊😊😊.
 - Needs complex numbers 😞 but worth it.

Summary (Irwin/Nelms Ch 8)

10: Sine waves and phasors

- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis
- CIVIL
- Impedance and Admittance
- Summary (Irwin/Nelms Ch 8)

- Sine waves are the only bounded signals whose shape is unchanged by differentiation.
- Think of a sine wave as the projection of a rotating rod onto the horizontal (or real) axis.
 - A *phasor* is a complex number representing the length and position of the rod at time $t = 0$.
 - If $V = a + jb = r\angle\theta = re^{j\theta}$, then
$$v(t) = a \cos \omega t - b \sin \omega t = r \cos(\omega t + \theta) = \Re(Ve^{j\omega t})$$
 - The *angular frequency* $\omega = 2\pi f$ is assumed known.
- If **all sources in a linear circuit are sine waves having the same frequency**, we can use phasors for circuit analysis:
 - Use complex impedances: $j\omega L$ and $\frac{1}{j\omega C}$
 - Mnemonic: CIVIL tells you whether I leads V or vice versa (“leads” means “reaches its peak before”).
 - Phasors eliminate time from equations 😊, converts simultaneous **differential** equations into simultaneous **linear** equations 😊😊😊.
 - Needs complex numbers 😞 but worth it.