

Fig (a)



Fig (b)

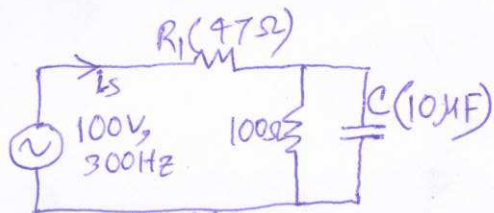


Fig (c)

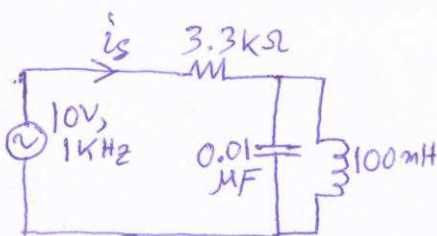


Fig (d)

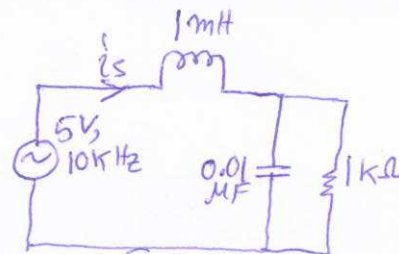


Fig (e)

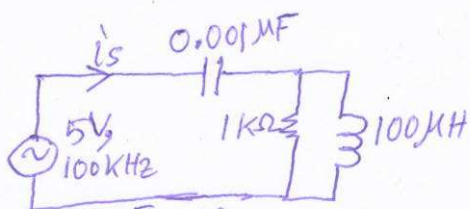


Fig (f)

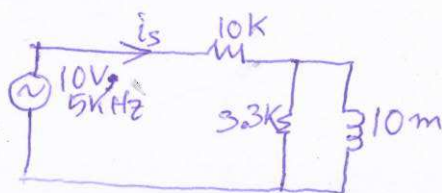


Fig (g)

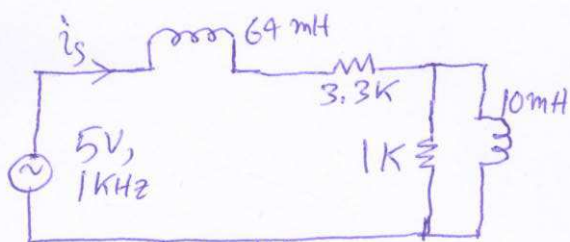


Fig (h)

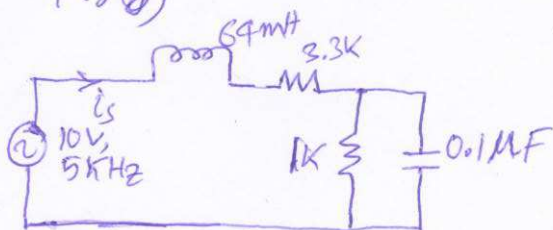


Fig (i)

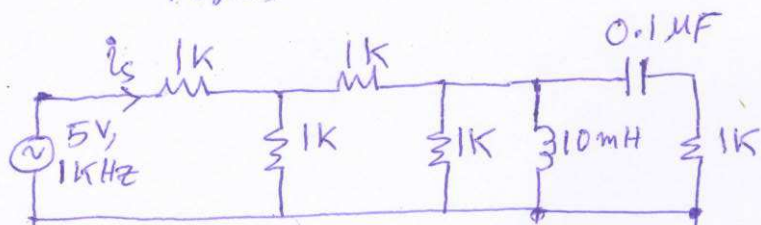


Fig (j)

1. Write the differential equation for supply current i_s and solve it. Assume initial conditions are zero.
2. Calculate the constants of the solution and derive the complete response.
3. Analyze the circuit to determine i_s , voltage across all elements, and the phase angle of all these voltages and i_s with respect to the supply voltage e_s . Draw the phasor diagram.
4. Write the state-equation(s) for the circuit. In case of R-L-C circuits, calculate the Eigen values from the matrix **A**.